


Bandpass-Band Reject (Bp-Br) Cavity Resonators

- Simulations vs Measurements
- Impedance plots showing how it works


Jacques Audet
June 2017
ve2azx.net

Circuit used for simulating the Bp-Br Cavity Resonator

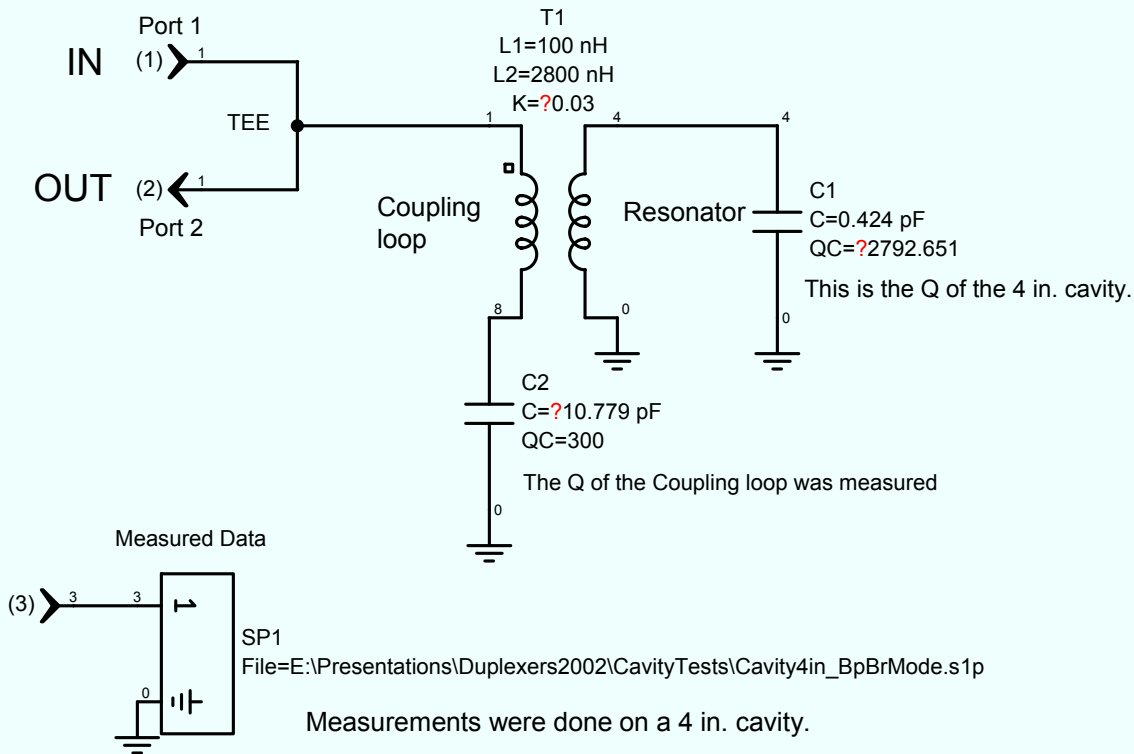
Value of C2, Coupling K and C1 Q factor were adjusted to match measured data at the bandpass and notch frequencies.



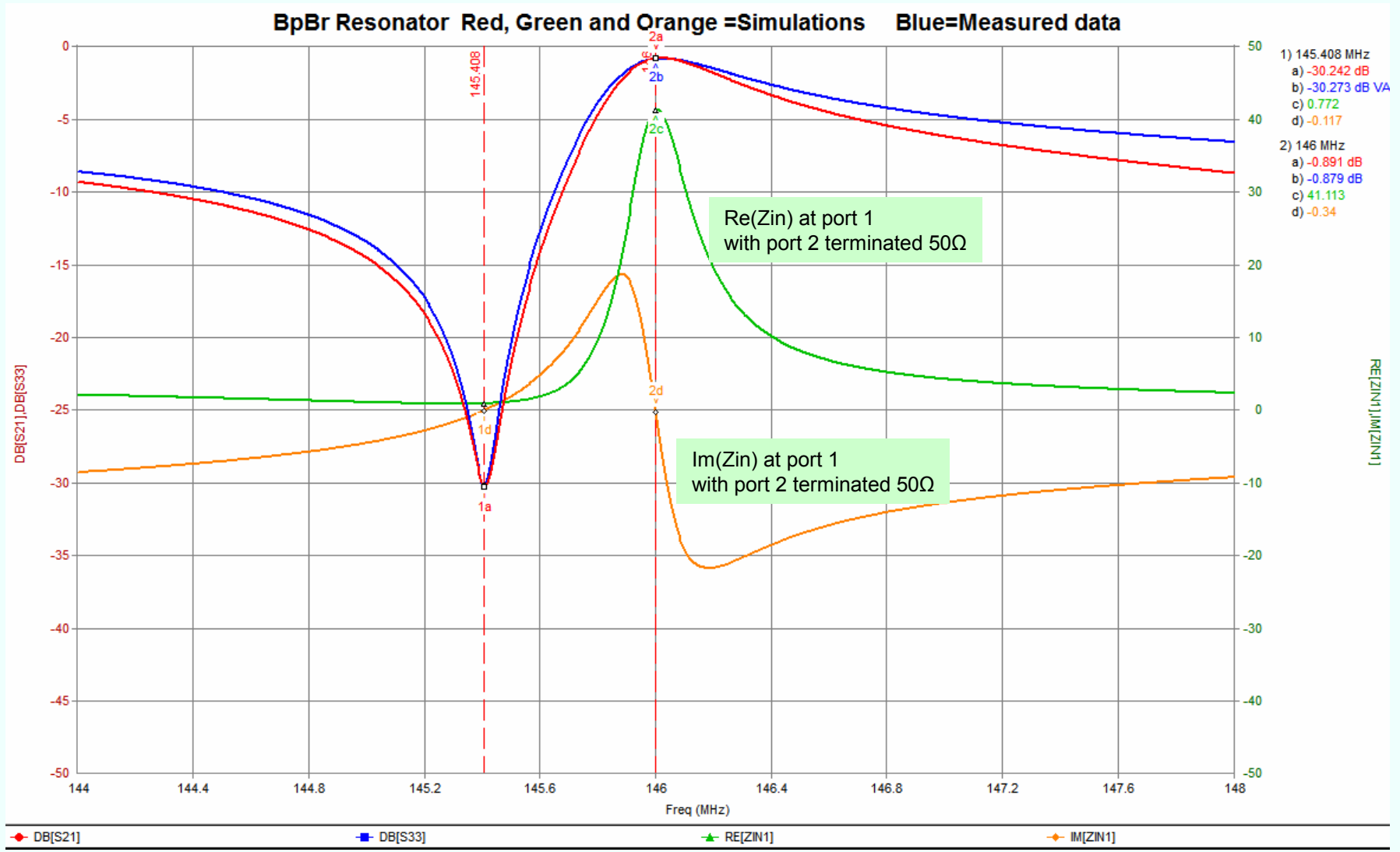
Note: Although the simulation s/w uses one port, it's really the measured S21. See the blue curve next sheet.



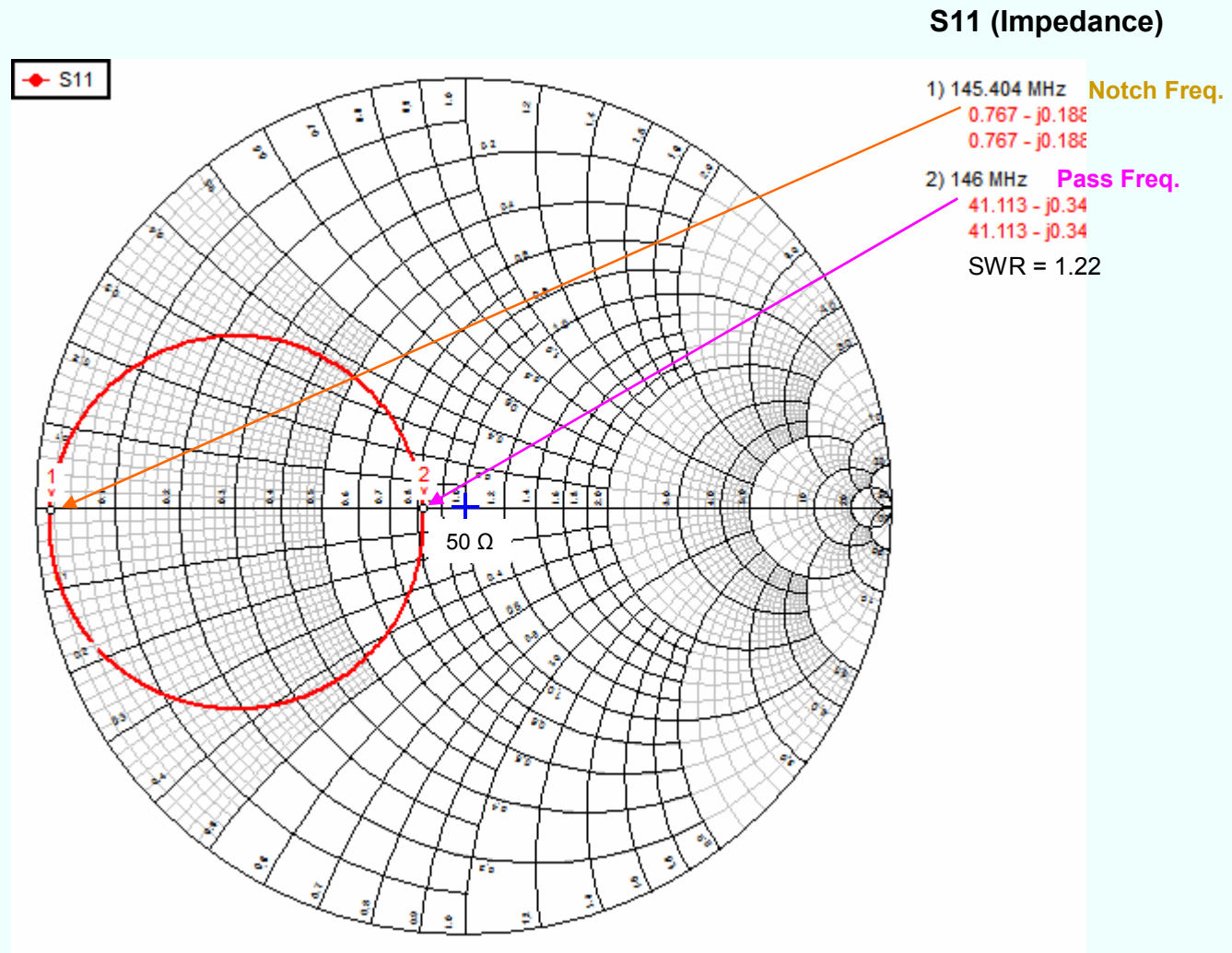
As seen at the Tee IN – OUT, with one side terminated in 50Ω



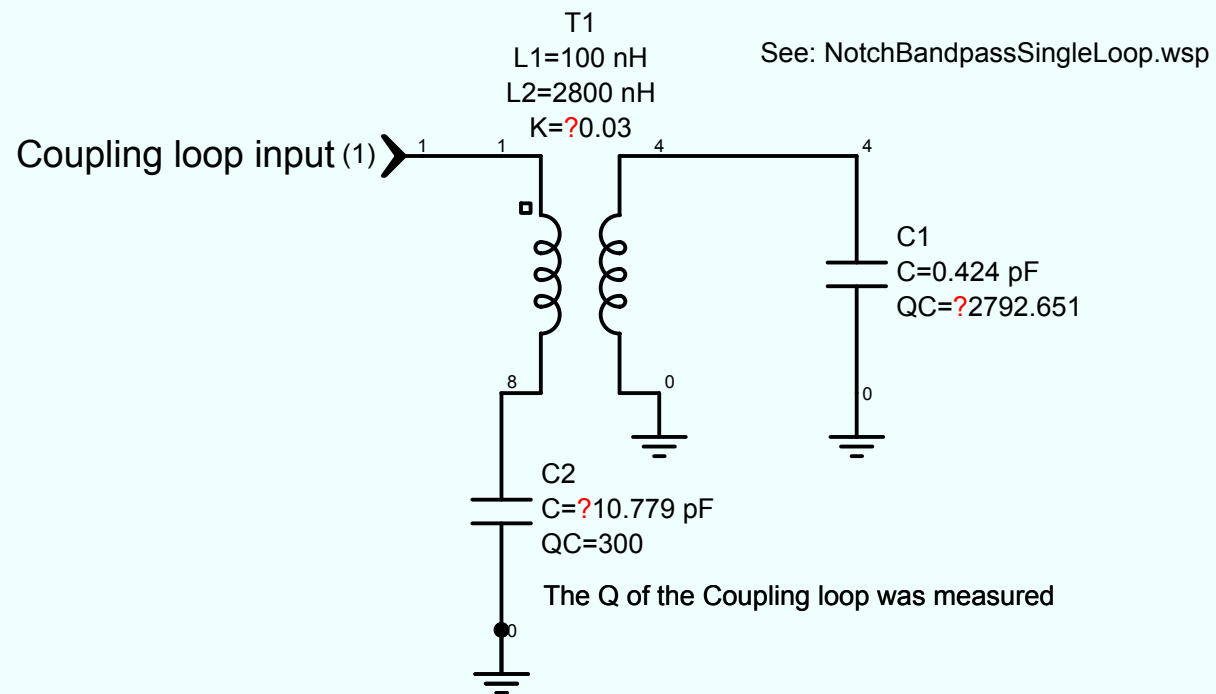Impedance seen at the coupling loop, based on the previous circuit (page 2)




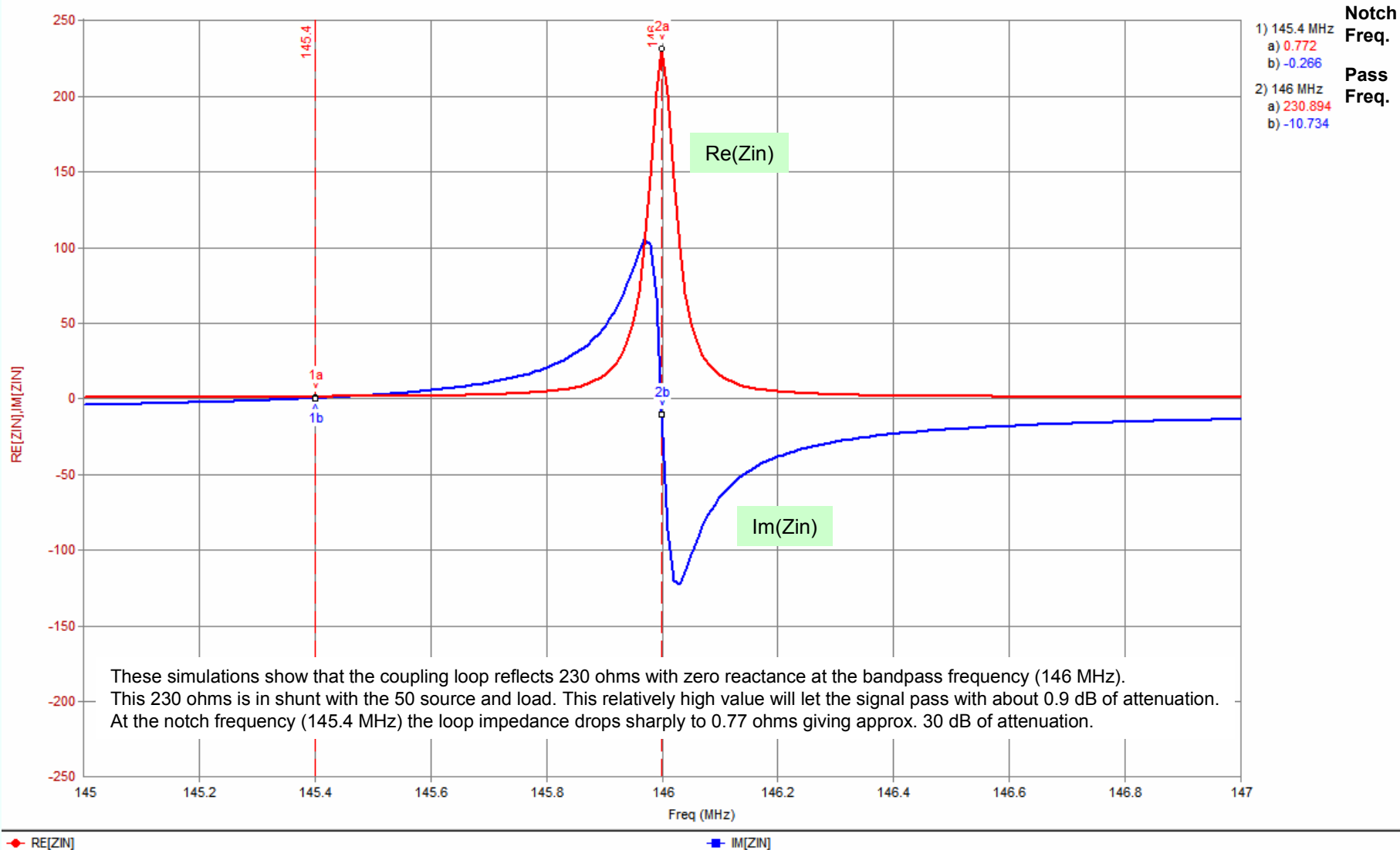Complex impedance seen at the Coupling loop input



These simulations show that the coupling loop reflects 230 ohms with zero reactance at the bandpass frequency (146 MHz). This 230 ohms is in shunt with the 50 source and load. This relatively high value will let the signal pass with about 0.9 dB of attenuation. At the notch frequency (145.4 MHz) the loop impedance drops sharply to 0.77 ohms giving approx. 30 dB of attenuation.

As seen at the coupling loop input

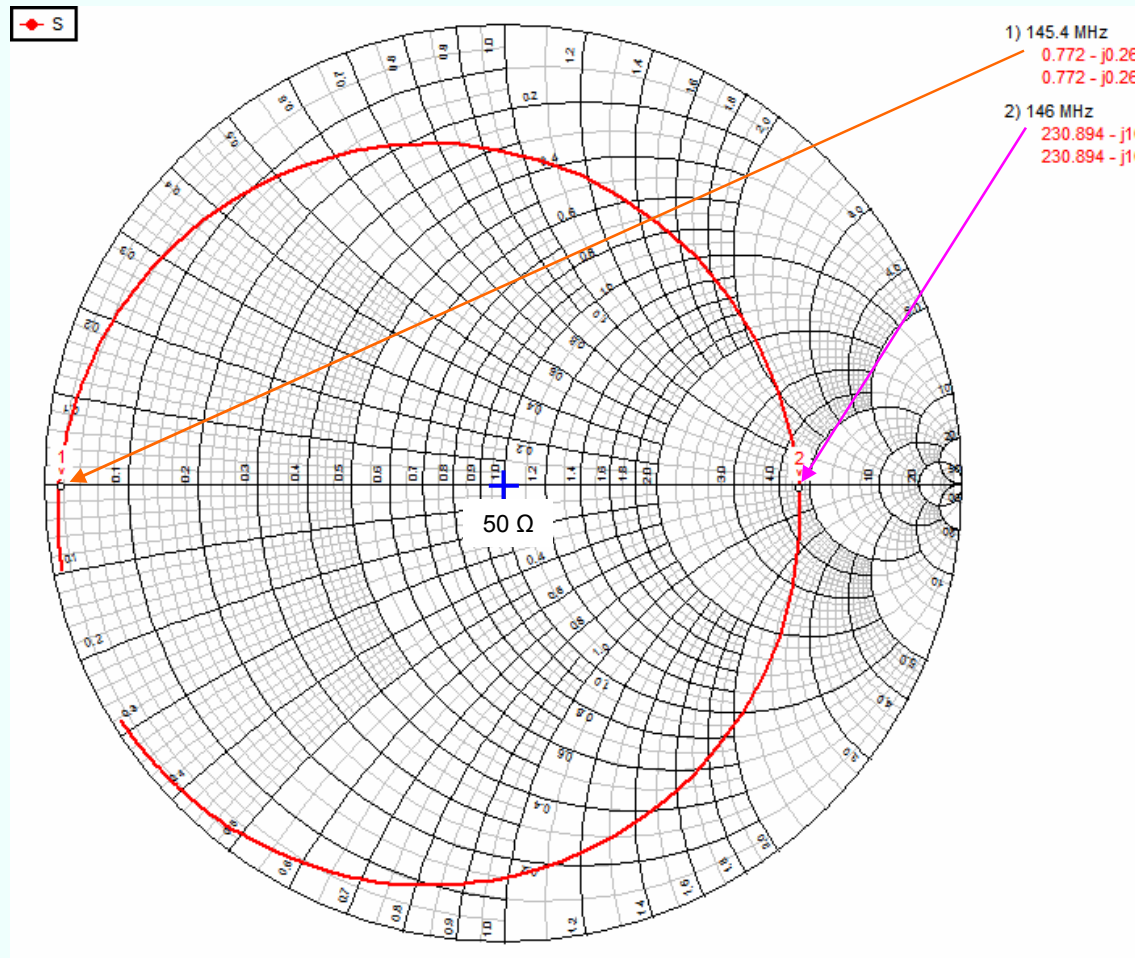

Notch Freq.

Pass Freq.

Coupling loop tests
Q Factor of 4 in. Cavity Loop - Bp-Br mode

See: http://ve2azx.net/technical/Calc_Series-Par_RLC.xls

For this test, the cavity is opened, leaving the coupling loop exposed, without the cylinder.

SERIES MODE RESULTS	
SERIES Ls in nH	103.50
SERIES Cs in pF	10.72
SERIES Rs ohms	0.330
SERIES Xs ohms	98.266


Q FACTOR =	298.14
3 dB BANDWIDTH (KHz)	507
CALC. RESONANT FREQ in MHz	151.1028
% OFF FROM MEAS. RESONNANCE	-0.038



Note that the series Rs of the coupling loop alone is 0.33 Ω
When it is used as part of the Bp-Br cavity it is 0.77 Ω .


Cascading TWO Bp-Br cavities interconnected with a quarter wavelength cable:

Simulating the shunt resistances at the notch frequency.

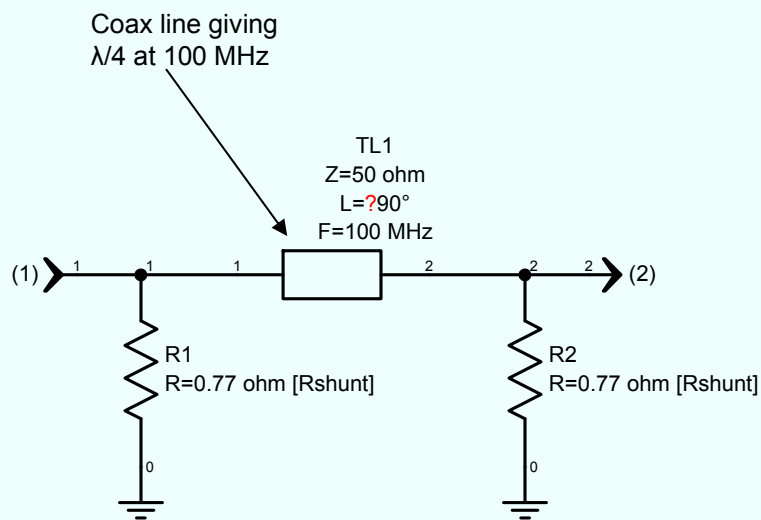


The 0.77 ohm resistors are the shunt resistance at the notch freq of 2 resonators
 Addind a quarter wavelength increases the losses 26 dB (at 100, 300 MHz)

See: NotchBandpassSingleLoop.wsp

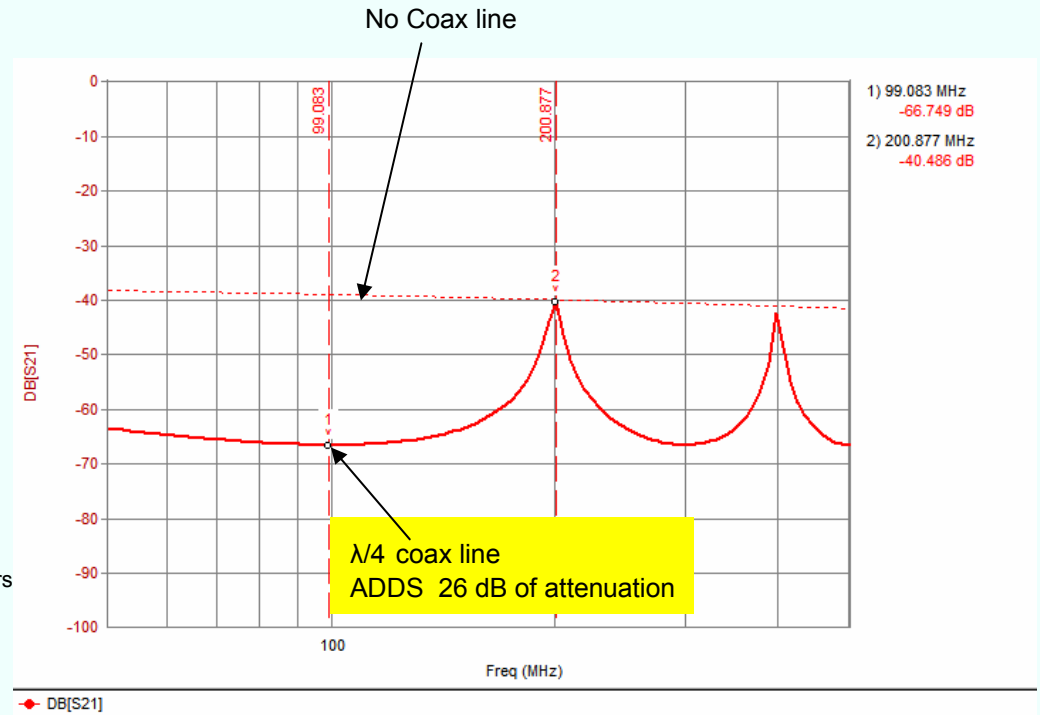


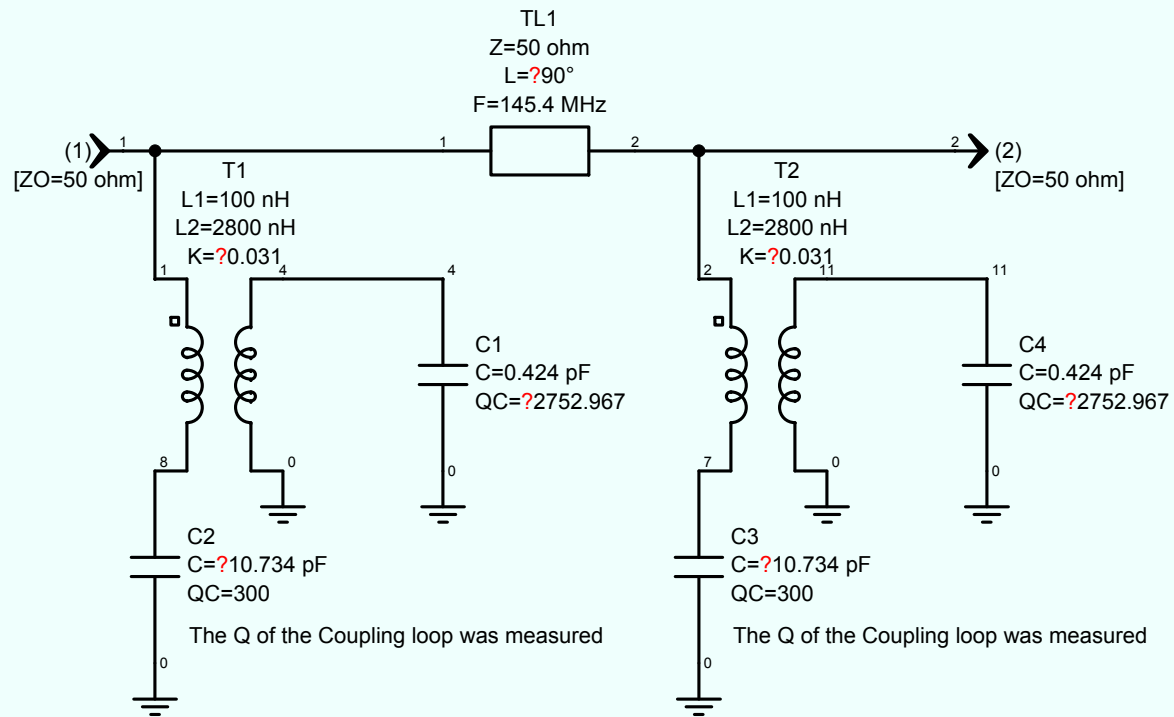Cascading TWO Bp-Br cavities interconnected with a quarter wavelength cable:




Cascading TWO Bp-Br cavities interconnected with a quarter wavelength cable:

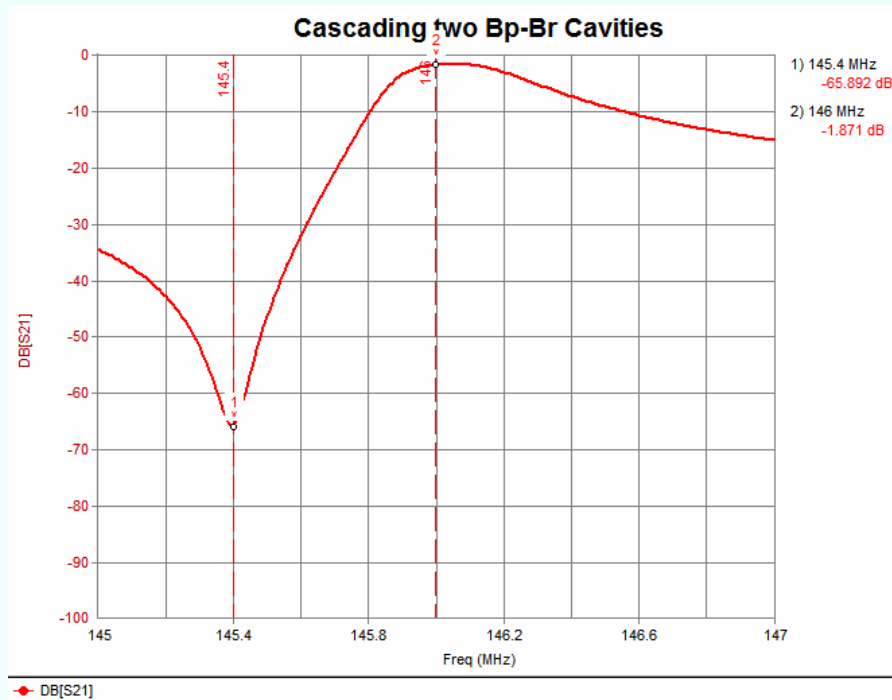The notch depth increases by ~26 dB with the 2nd cavity
 Insertion loss is now 1.87 dB.
 Was 0.8 dB with one cavity. See page 3.



Input impedance at port 1

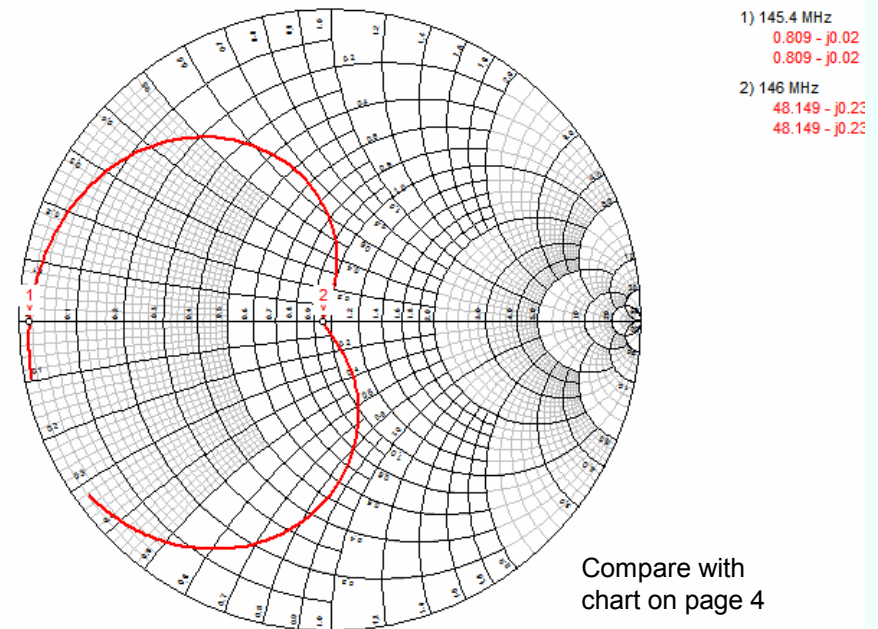

Total notch depth with 2 cavities = 6 dB + Notch depth of one cavity in dB x 2
 (assuming the cavities have similar notch depths)