

DMMCheck Plus Voltage Reference

J. Audet
Dec 2013


Factory calibration.

$R_s := 25$ Source resistance

$R_v := 10^7$ DMM calibration resistance

$E_o := 5$ Cal value

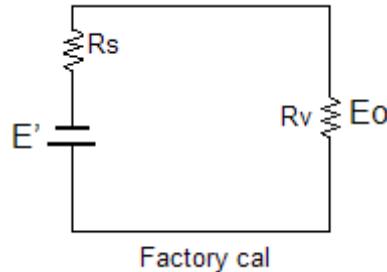E' is adjusted to read $E_o = +5.0000 \text{ V}$




Re - calibration with divider, with load R_v

E is re-adjusted to read $E_o = +5.0000 \text{ V}$

$R_1 := 100.04$ $R_2 := 1000.78$

$R_3 := 10002$ $R_4 := 100096$

$R := R_1 + R_2 + R_3 + R_4$

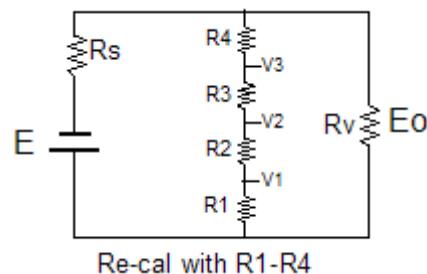

$$E_o = E \cdot \frac{\frac{R_v \cdot R}{R_v + R}}{\frac{R_v \cdot R}{R_v + R} + R_s}$$

$$E_o = R \cdot R_v \cdot \frac{E}{(R_v \cdot R + R_s \cdot R_v + R_s \cdot R)} \quad \text{Eq. 1}$$

Solve for E :

$$E := \frac{E_o}{R \cdot R_v} \cdot (R_v \cdot R + R_s \cdot R_v + R_s \cdot R) \quad \text{Eq. 2}$$

$E = 5.001137$ New E value to read $E_o = +5.0000 \text{ V}$

The thevenin resistance of source E is $\sim R_s$, since R and $R_v \gg R_s$


E_{o1} with a different load: R_{v1} , the voltmeter resistance

$R_{v1} := 10^6$

$$R_{Th4} := \frac{R \cdot R_s}{R + R_s} \quad R_{Th4} = 24.994 \quad \begin{matrix} \text{Eq. 3} \\ \text{Thevenin resistance} \end{matrix}$$

$$V_{Th4} := E \cdot \frac{R}{R + R_s} \quad V_{Th4} = 5.000012 \quad \begin{matrix} \text{Eq. 4} \\ \text{Open circuit voltage} \end{matrix}$$
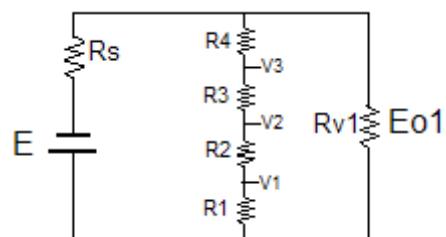
$$E_{o1} := V_{Th4} \cdot \frac{R_{v1}}{R_{v1} + R_{Th4}} \quad E_{o1} = 4.999888 \quad \begin{matrix} \text{Eq. 5} \\ \text{Voltage at } E_{o1} \end{matrix}$$



Voltage at V3, with RV1 connected at V3:

$$R_{Th3} := \frac{(R1 + R2 + R3) \cdot (R4 + Rs)}{R + Rs}$$

Eq. 7
Thevenin resistance

$$R_{Th3} = 9994.491$$

$$V_{Th3} := E \cdot \frac{(R1 + R2 + R3)}{R + Rs}$$

Eq. 8
Open circuit voltage

$$V_{Th3} = 0.499234$$

$$V3 := V_{Th3} \cdot \frac{Rv1}{Rv1 + R_{Th3}}$$

Eq. 9
Voltage at V

$$V3 = 0.494294$$

Voltage at V2, with RV1 connected at V2:

$$R_{Th2} := \frac{(R1 + R2) \cdot (R3 + R4 + Rs)}{R + Rs}$$

Eq. 10
Thevenin resistance

$$R_{Th2} = 1089.925$$

$$V_{Th2} := E \cdot \frac{(R1 + R2)}{R + Rs}$$

Eq. 11
Open circuit voltage

$$V_{Th2} = 0.049498$$

$$V2 := V_{Th2} \cdot \frac{Rv1}{Rv1 + R_{Th2}}$$

Eq. 12
Voltage at V2

$$V2 = 0.049444$$

Voltage at V1, with RV1 connected at V1:

$$R_{Th1} := \frac{(R1) \cdot (R2 + R3 + R4 + Rs)}{R + Rs}$$

Eq. 13
Thevenin resistance

$$R_{Th1} = 99.95$$

$$V_{Th1} := E \cdot \frac{(R1)}{R + Rs}$$

Eq. 14
Open circuit voltage

$$V_{Th1} = 0.004498$$

$$V1 := V_{Th1} \cdot \frac{Rv1}{Rv1 + R_{Th1}}$$

Eq. 15
Voltage at V1

$$V1 = 0.004498$$


Effect of Input Capacitance at AC 100 Hz on V3 voltage

$$y(x) := -9.848127 \cdot 10^{-7} \cdot x + 0.4939582$$

From Rdg vs pF.xls

$$y = -9.848127E-07x + 4.939582E-01$$

$$x := 0, 1..160$$

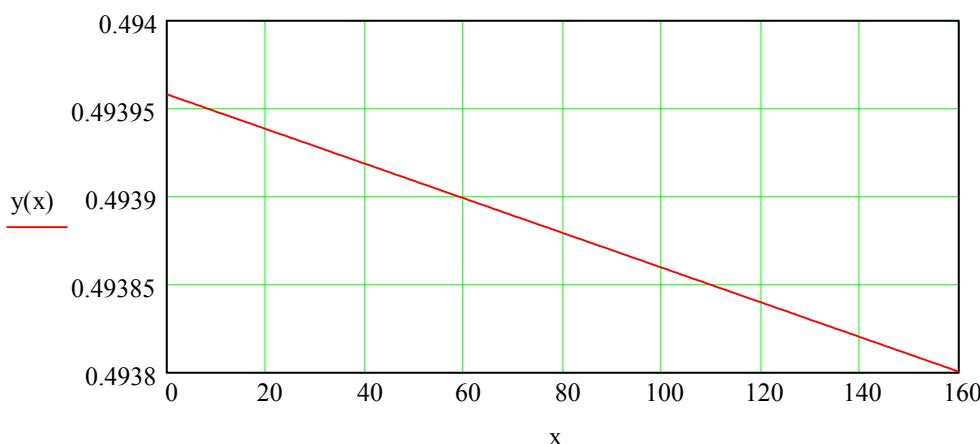

$$y(60) = 0.4939$$


$$y(x) := -9.848127 \cdot 10^{-7} \cdot x + 0.4939582$$

$$Y(x) := \frac{-9.848127 \cdot 10^{-7}}{y(0)} \cdot x + \frac{0.4939582}{y(0)}$$

$$\frac{-9.848127 \cdot 10^{-7}}{y(0)} = -1.993717 \times 10^{-6}$$

$$Y(x) := -1.993717 \times 10^{-6} \cdot x + 1$$

$$\frac{0.4939582}{y(0)} = 1$$

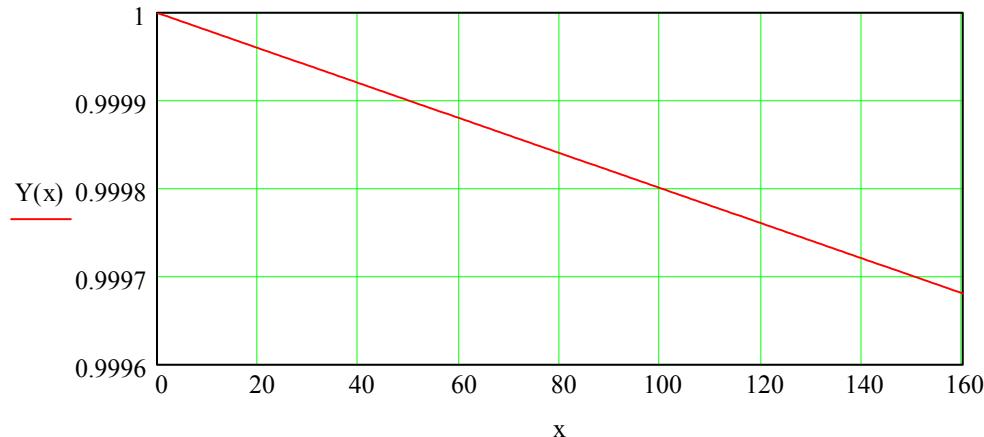

Changed the sign of the slope

$YY(x)$ is the mult factor to use to correct for the input capacitance

$$YY(x) := \frac{9.848127 \cdot 10^{-7}}{y(0)} \cdot x + \frac{0.4939582}{y(0)} \quad \frac{0.4939582}{y(0)} = 1$$

$$YY(x) := 1.994 \cdot 10^{-6} \cdot x + 1$$

