

# HP 4342A Q Meter Tests


S/N: 1212J01342

Jacques Audet VE2AZX  
ve2azx.net  
Mar 1 2023



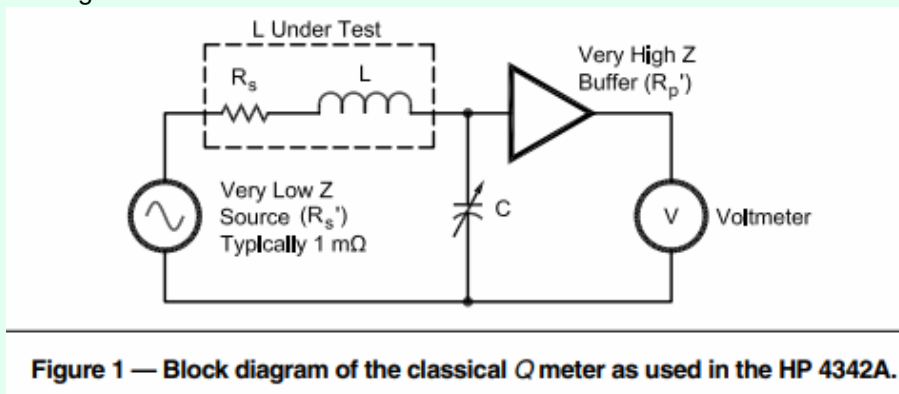
## Intent of this Document

- Describe how I measured the important parameters of the HP4342A Q Meter and provide results.
- This is the classical instrument for measuring the Q factor, that I am fortunate to own.
- Will show how to build a low output impedance transformer, similar to the HP Q meter, giving a very low impedance.
- Will show how to correct the decrease in Q reading caused by the source resistance. (Excel sheet)  
For both HP4342A and Boonton 260A
- This complements my QEX article on Q factor measurements:  
See: [http://ve2azx.net/technical/Q-FactorMeas\\_on\\_LC\\_Circuits.pdf](http://ve2azx.net/technical/Q-FactorMeas_on_LC_Circuits.pdf)  
and figure 1 below.



## Block Diagram of the HP4342A Q Meter

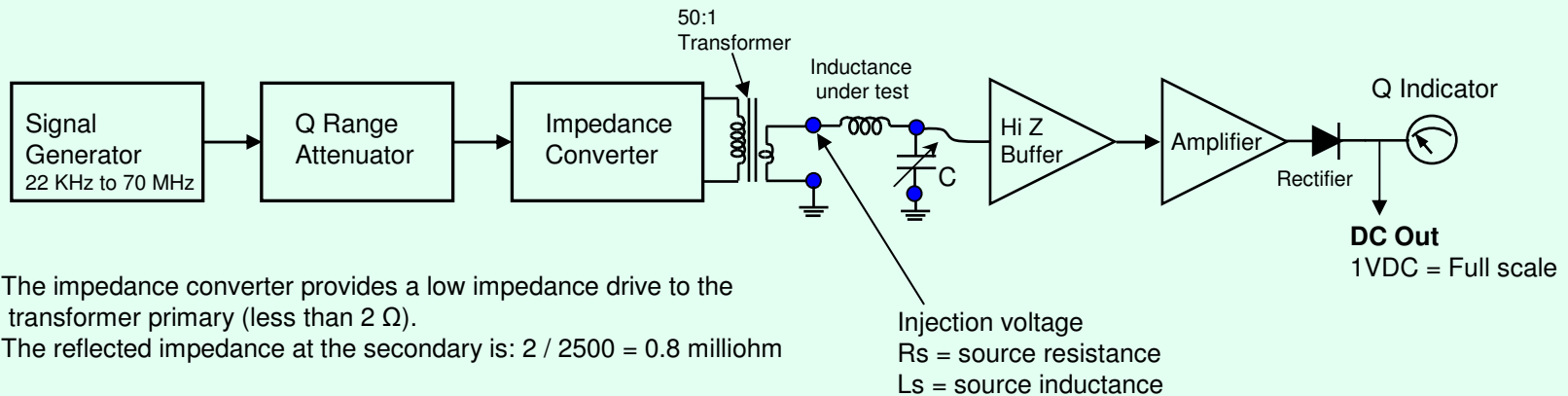

The impedance converter provides a low impedance drive to the transformer primary (less than 2  $\Omega$ ).  
 The reflected impedance at the secondary is:  $2 / 2500 = 0.8$  milliohm

The injection voltage varies with the Q range as follows:

Q range	Injection V	dBm (50 $\Omega$ )
30	30 mV (as calibrated)	-17.45
100	9 mV	-27.90
300	3 mV	-37.45
1000	0.9 mV	-47.90

The Q Range attenuator must adjust levels according to the Q range selected.  
 To go from a Q range of 30 to 100 requires a level change of  $100/30 = 3.333$   
 Attenuation in dB =  $20 * \log(3.333) = 10.46$  dB


To go from a Q range of 100 to 300 requires a level change of  $300/100 = 3.000$   
 Attenuation in dB =  $20 * \log(3.000) = 9.54$  dB

Note that to go from a Q range of 30 to 300 requires a level change of  $300/30 = 10$   
 Attenuation in dB =  $20 * \log(10) = 20$  dB =  $10.46 + 9.54$

The calibration is done at 30 mV with the Q range set at 30.  
 This gives  $30 \text{ mV} \times 30 = 900 \text{ mV}$  full scale at the voltmeter input, on all Q ranges.  
 The voltmeter is adjusted to read 900 mV at 50 KHz.

## Measuring the Injection Source Flatness


At the transformer secondary

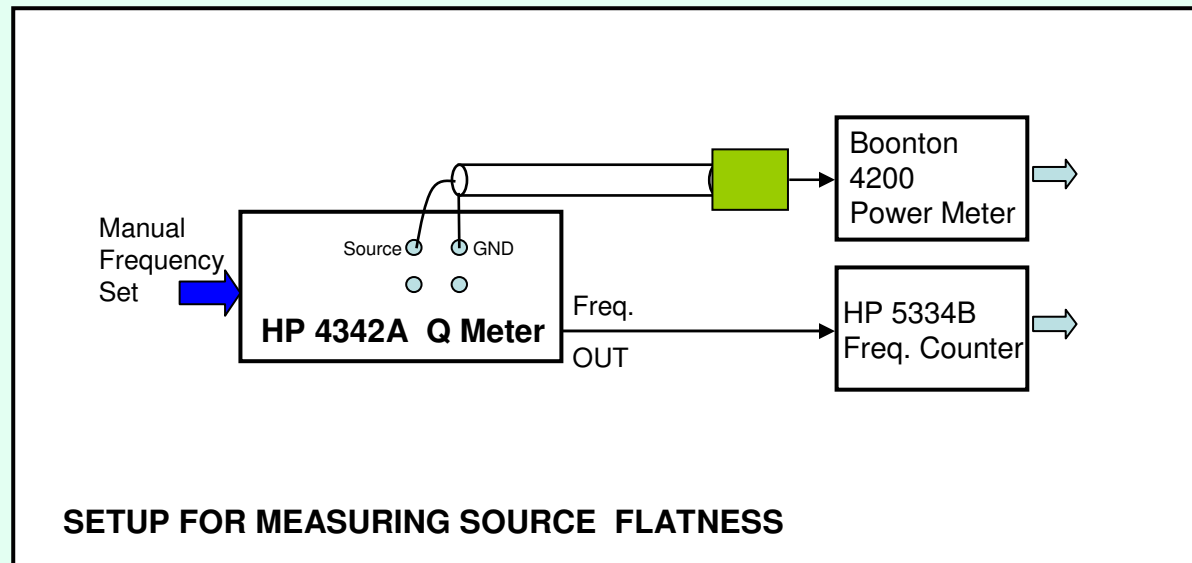



# Injection Source Flatness

Mostly automated test, using Labview

Ref: HP5334B-Boonton4200-V5A.vi

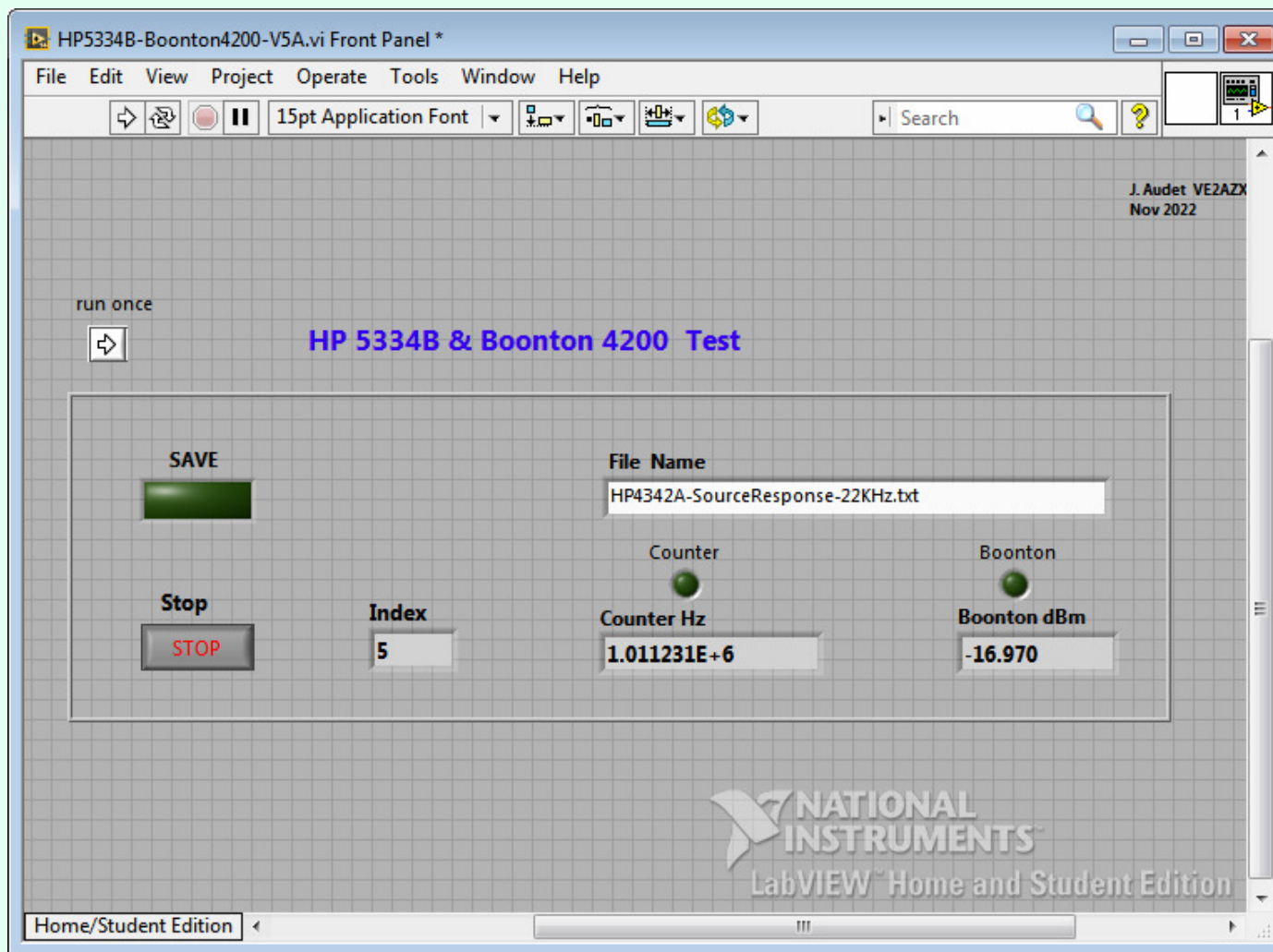


## Injection Source Flatness

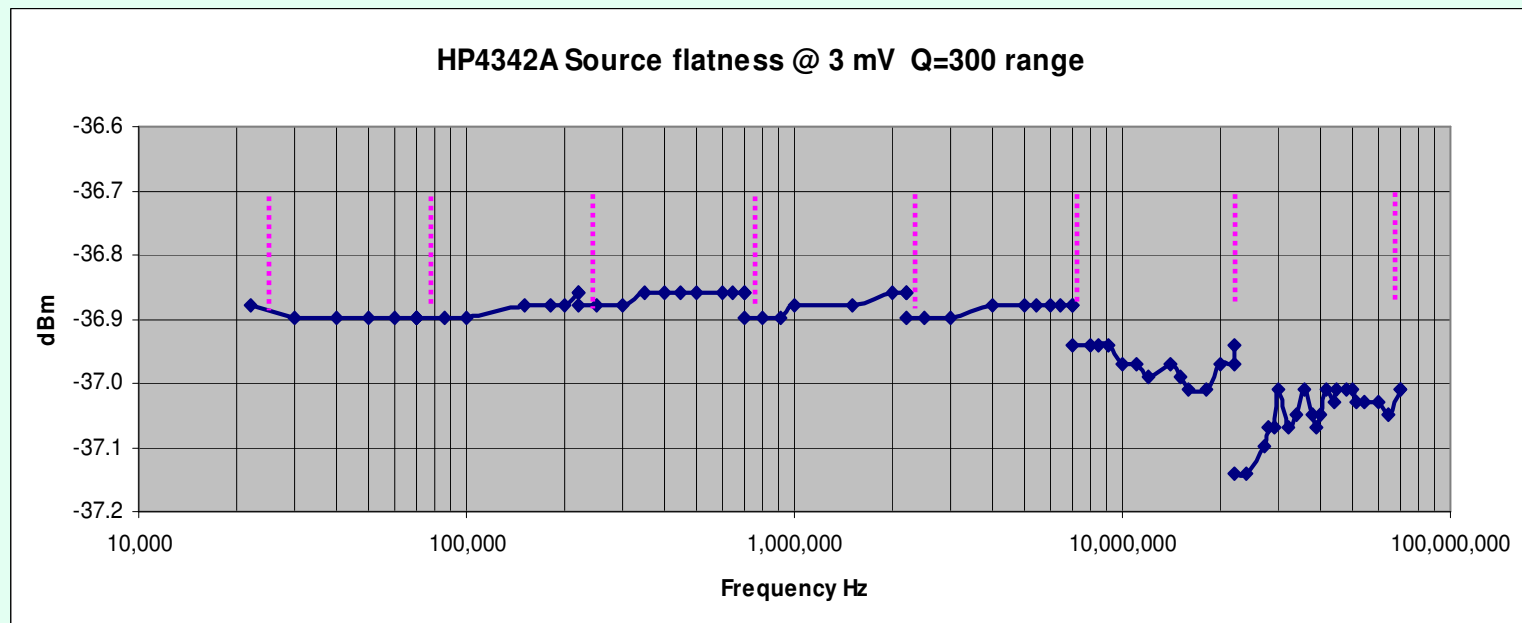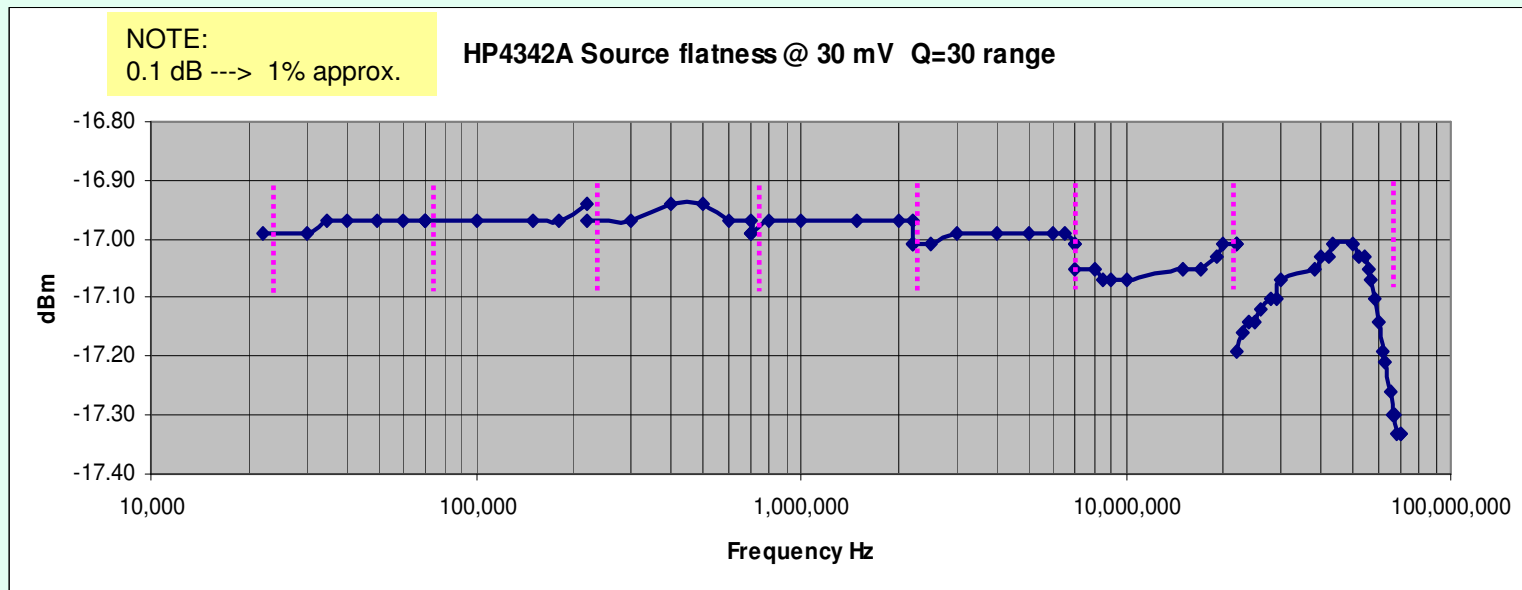


## Test of the Internal Q Range Attenuator

HP 4342A set at 100 KHz

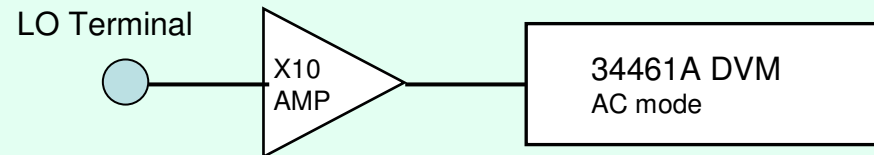


Q range	dB reading	Expected	Error
1000	0.00 Ref.	dB	dB
300	10.40	10.46	- 0.06
100	20.00	20.00	0.00
30	30.38	30.46	- 0.08
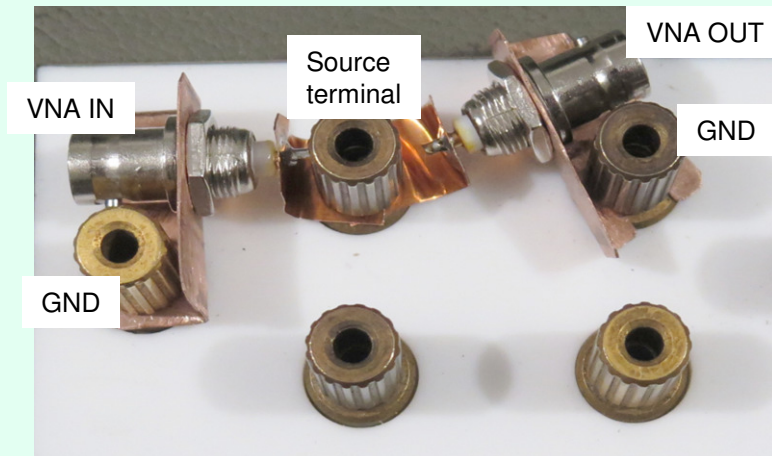
## Verification of the Source Resistance: $R_s$ and Inductance: $L_s$ (at the transformer secondary)



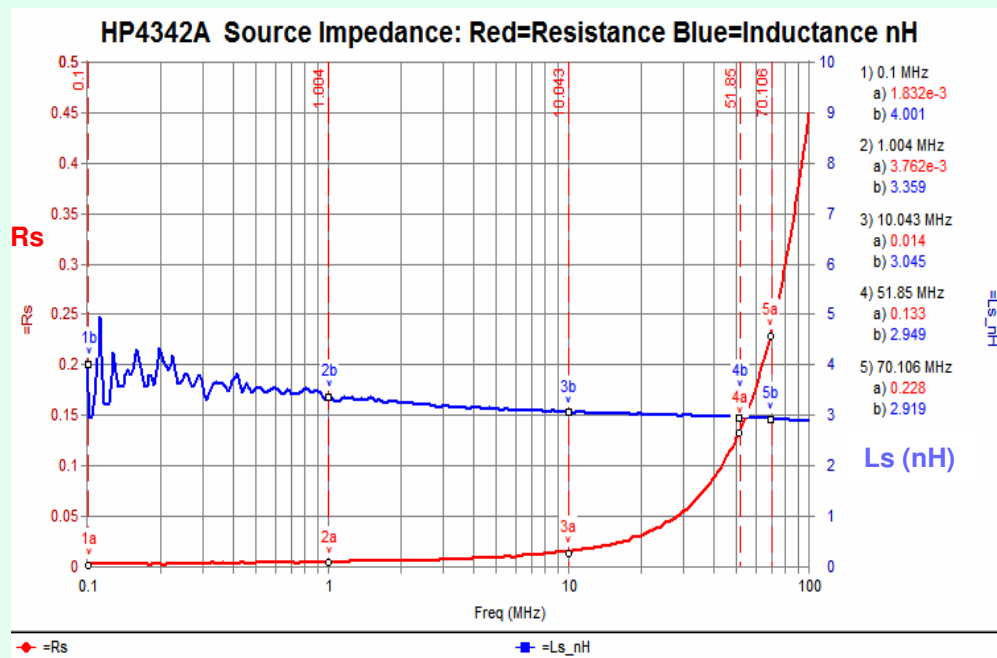- The tests are done in S21 mode with the unknown impedance connected in shunt. (across the source terminal)
- $R_s$  varies from 1.8 milliohm at 100 KHz, to 14 milliohm at 10 MHz, to 228 milliohm at 70 MHz. This comes from the transformer coupling coefficient which is below the ideal value of 1 (About 0.8)
- $L_s$  value is around 3 nH, (blue curve).



### ' SERIES and SHUNT IMPEDANCE CALCULATIONS

' S21 mode is used. Data from .s2p file  
 $Z_0=50$  ' Impedances of source and load.

$R = \text{RE}[S21]$  ' Extract Re and IM parts of measured S21.

$I = \text{IM}[S21]$

$C = \text{COMPLEX}(R, I)$  ' Convert to a complex number

' Select Z in SERIES connection. **Not Used.**

'  $Z = 2 * Z_0 * (1 - C) / C$  ' Calculate Z in serial mode.

' Select Z in SHUNT connection. **Used here.**

$Z = 0.5 * Z_0 * C / (1 - C)$  ' Calculate complex Z in shunt mode.

$\text{MagZ} = \text{MAG}(Z)$  ' Computes Impedance magnitude

$R_s = \text{RE}(Z)$  ' Series **Résistance**

$X_s = \text{IM}(Z)$  ' Series **Reactance**


$L_s_{\mu H} = X_s / (2 * \pi * \text{FREQ})$  ' FREQ in MHz

$L_s_{nH} = 1000 * L_s_{\mu H}$


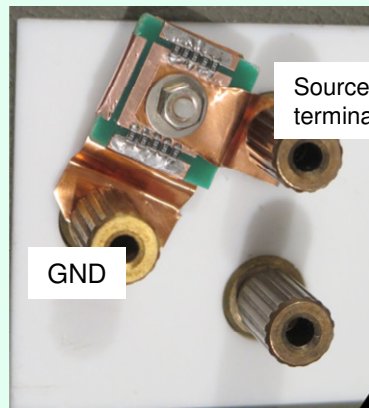
# Verification of the Impedance Converter and Transformer Response

Measured transformer turns ratio @ 100 KHz: 51




Source terminal

GND

0.1  $\Omega$  load used to test transmission (S21)

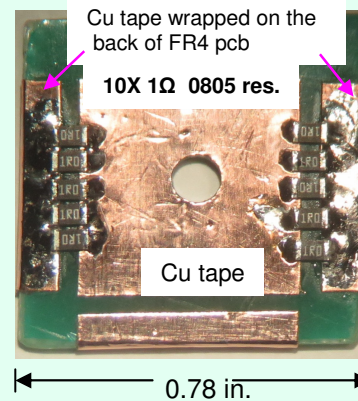0.1  $\Omega$  Resistor connected across source / gnd terminals




Cu tape wrapped on the back of FR4 pcb

10X 1 $\Omega$  0805 res.


Cu tape

0.78 in.

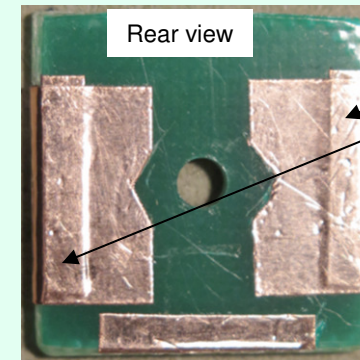


Rear view

Raised contact points

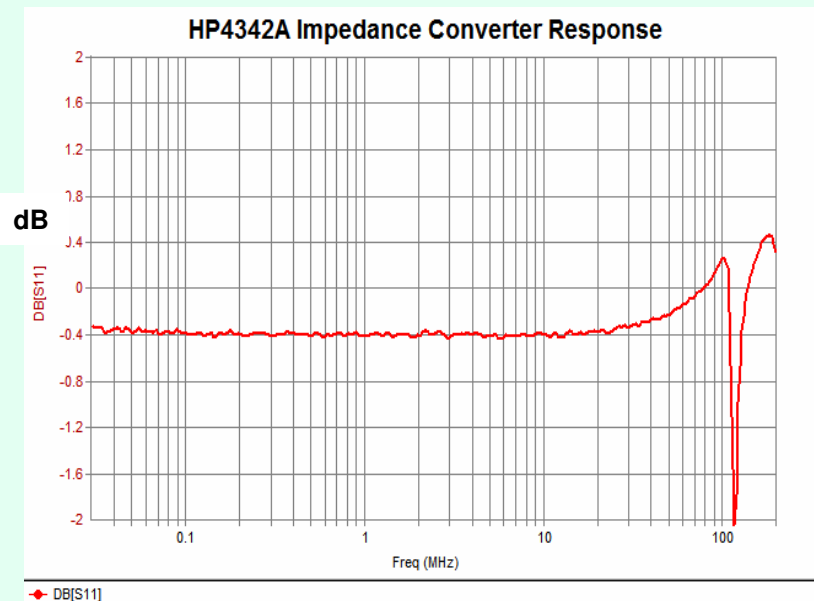

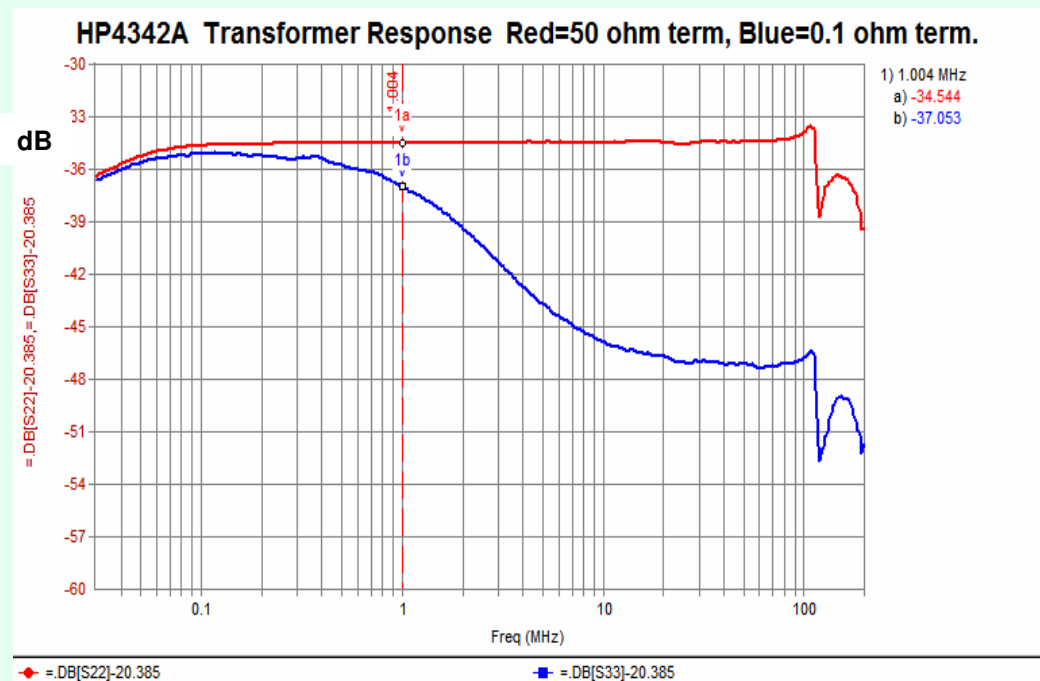It uses two emitter followers in cascade.




Note: Transformer response includes the impedance converter


9

Ref: HP4342A-Imped Cvtr and Xfrm Tests.wsp
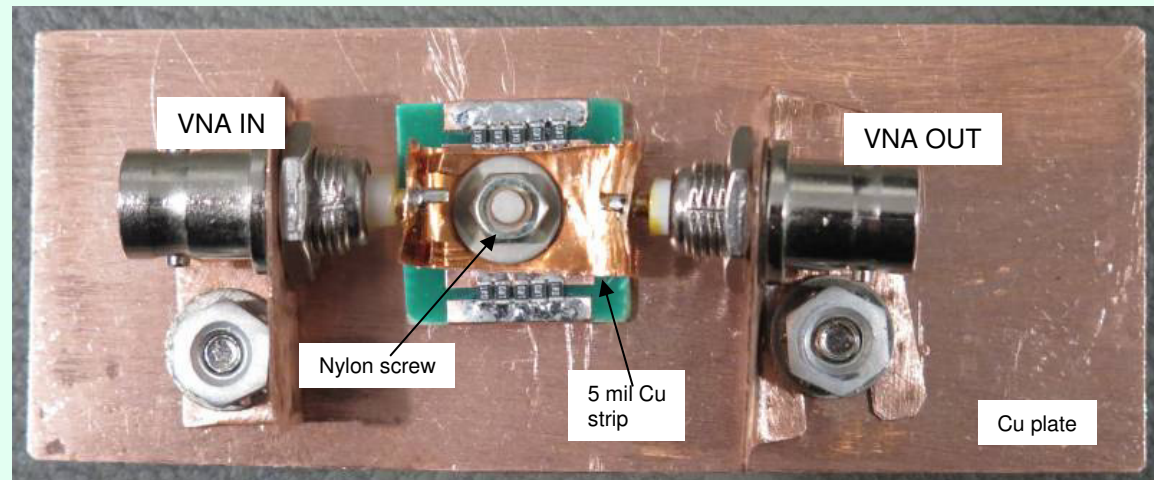
## Testing the Low Impedance 0.1 $\Omega$ Termination Resistor



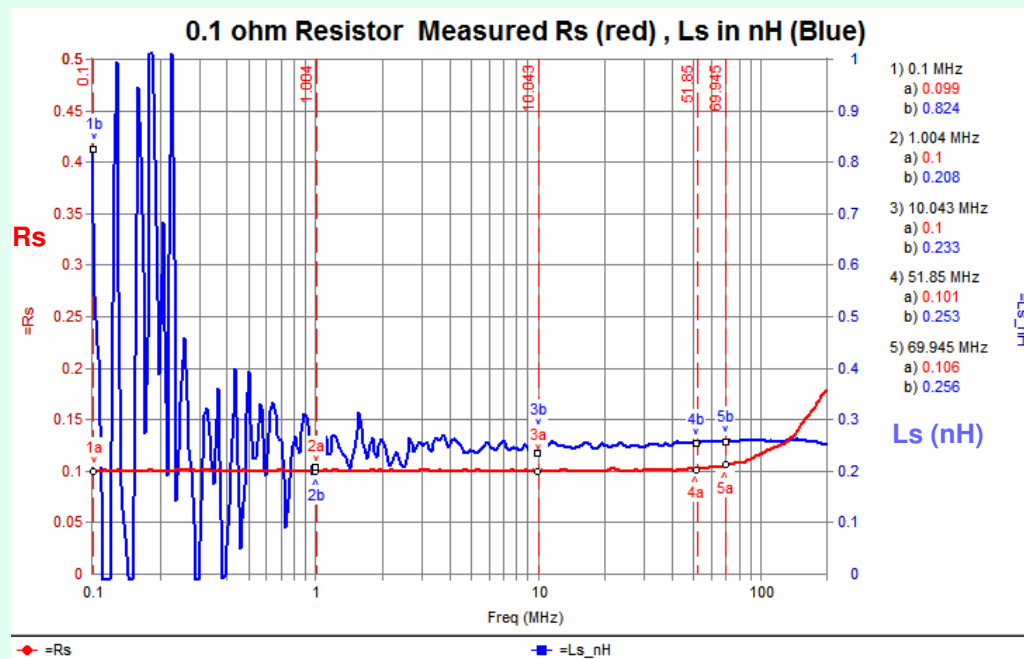
Set-up to measure the resistance  $R_s$  and inductance  $L_s$ , in S21 mode with shunt connection



- $R_s$  (red) is very constant up to  $\sim 70$  MHz at 0.1  $\Omega$
- $L_s$  (blue) varies slightly between 0.20 and 0.25 nH  
Such a small value is difficult to measure below 1 MHz ( $X_L = 1.6$  milli $\Omega$  at 1 MHz).


## Simulations of Impedance Converter (Transformer Driver).

For four different Transistors.


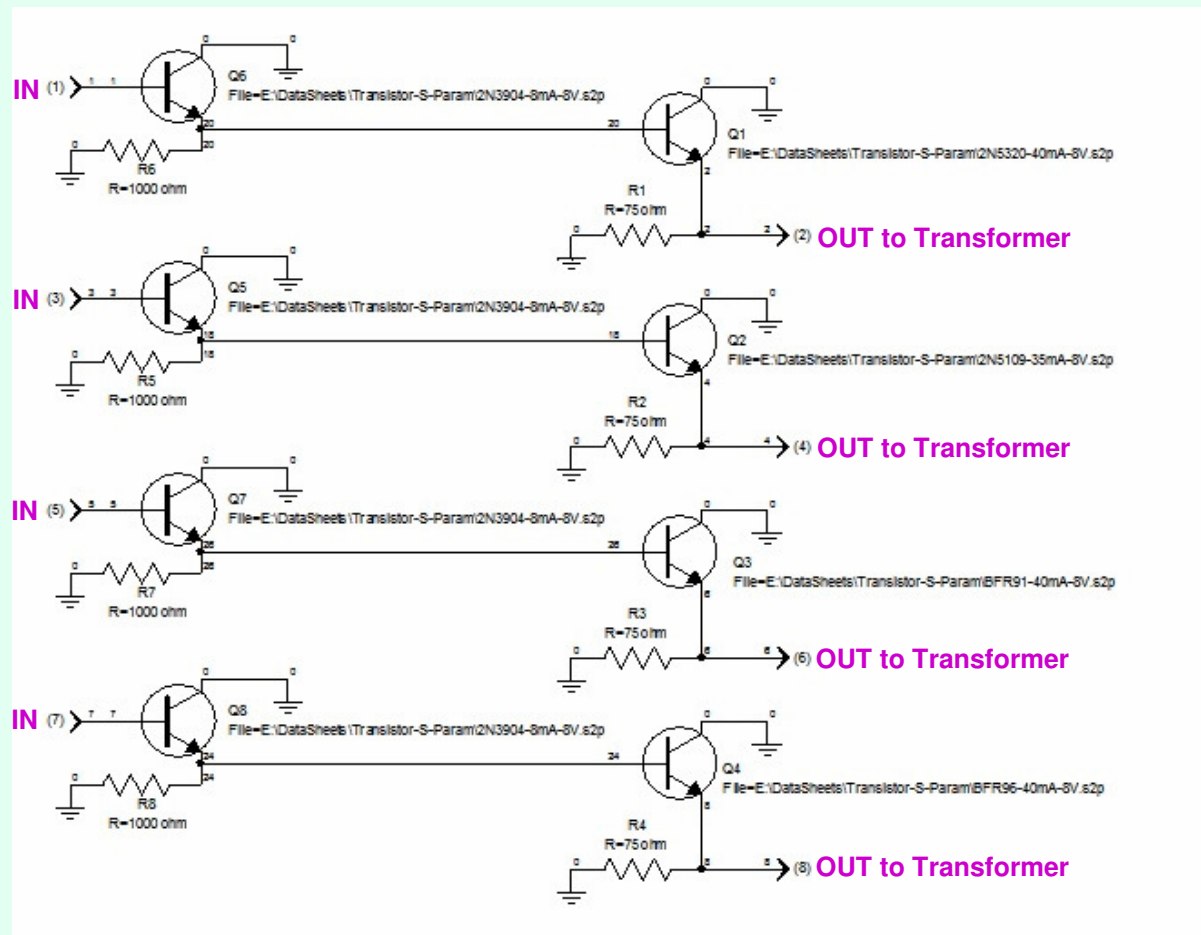


## Simulations of Impedance Converter Output Impedance


Using four different output transistors.

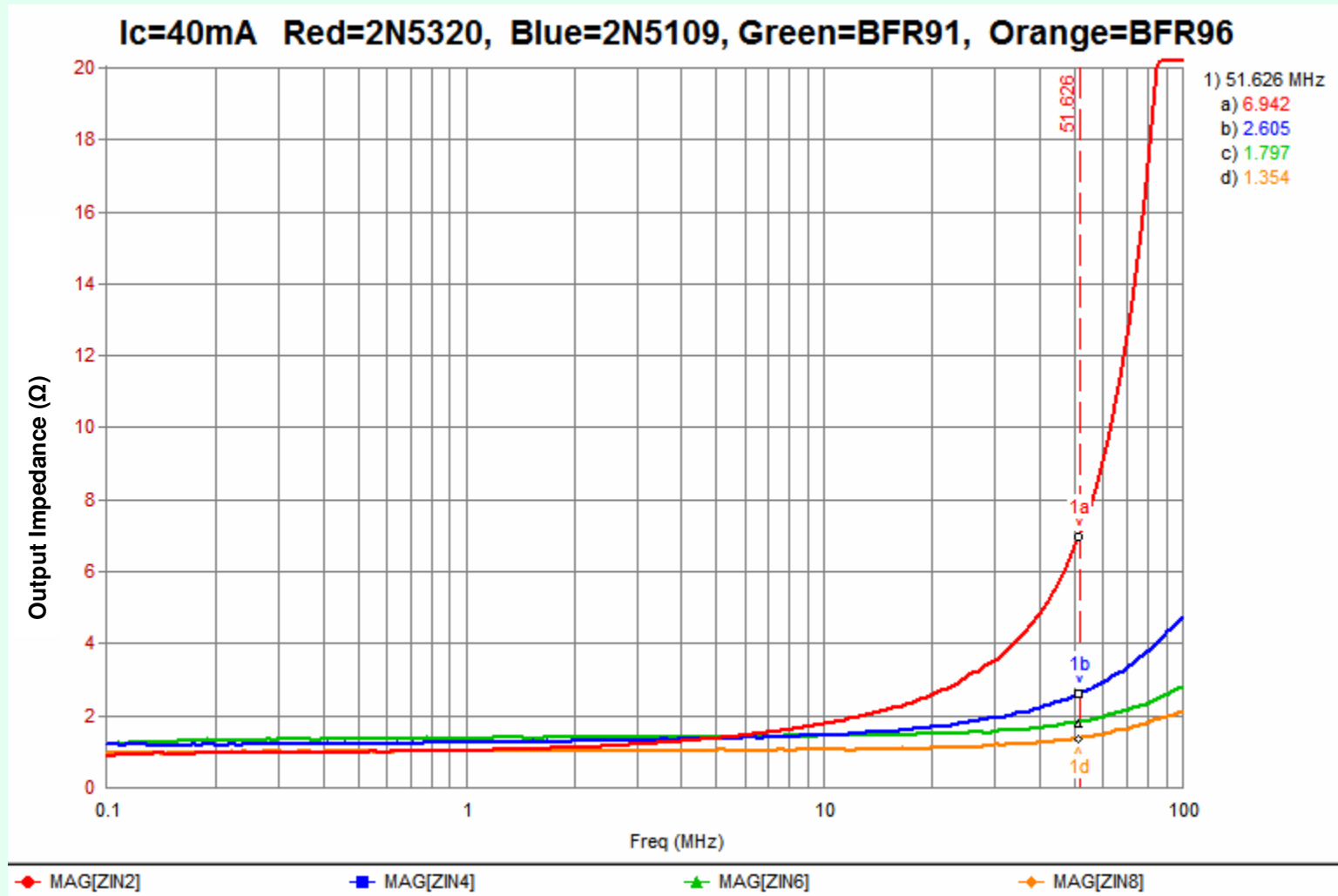
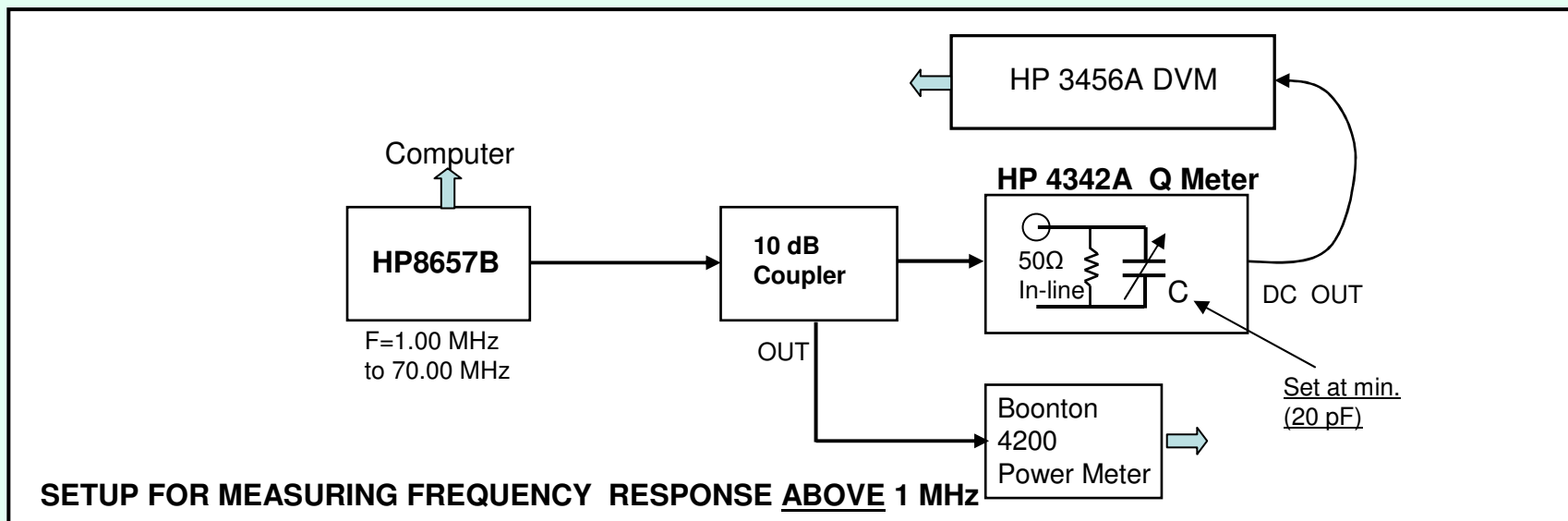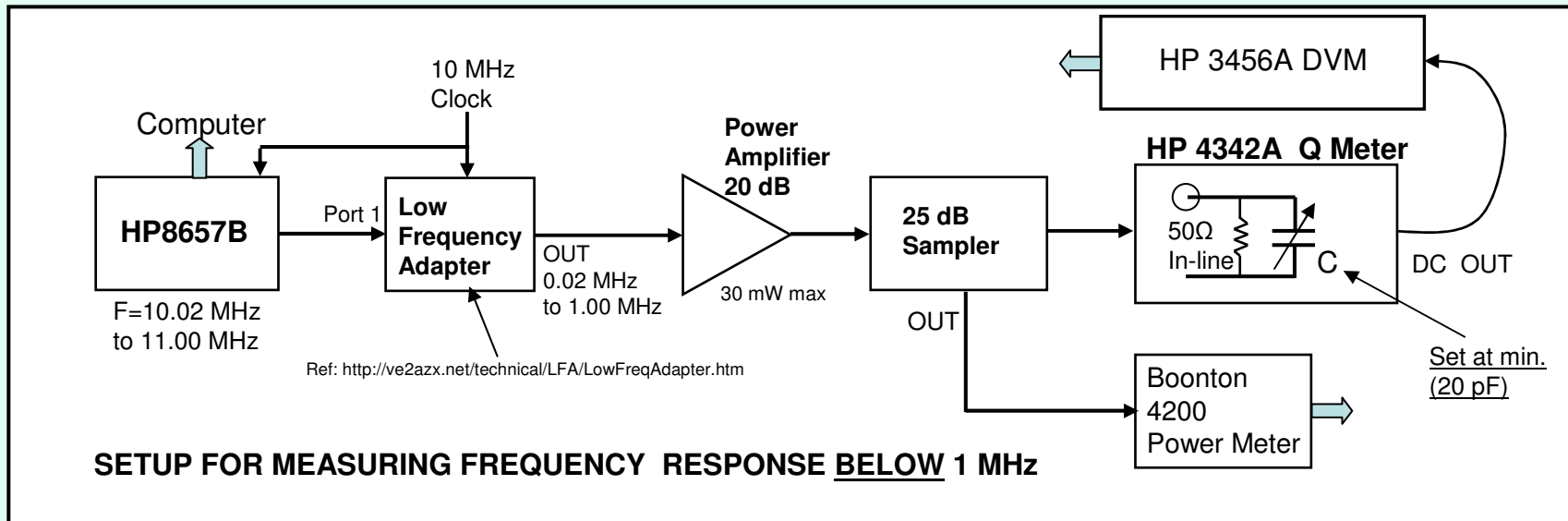
## Measuring the HP4342A Voltmeter Frequency Response



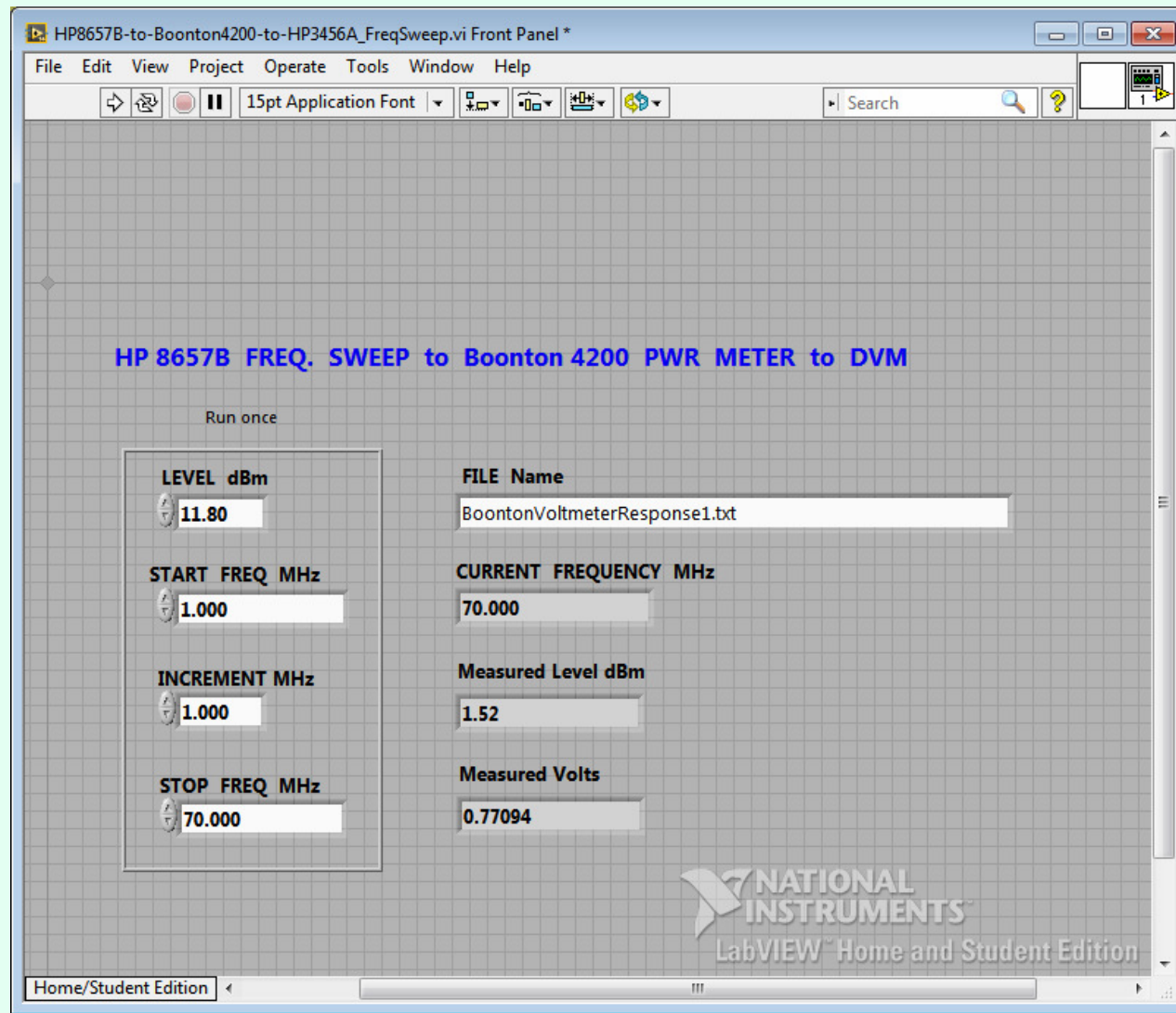
## Measuring the Q Voltmeter Frequency Response Using Labview to automate the measurements




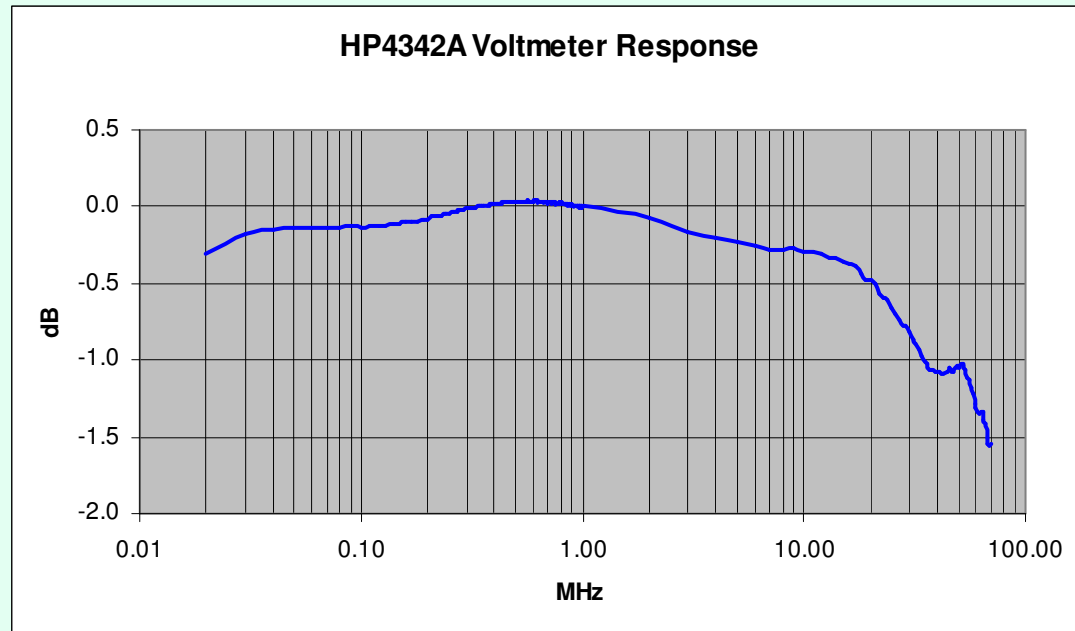**Before adjustments**

**Note:** 0.5 dB = 6%  
1 dB = 12%  
1.5 dB = 19%




**After adjustments**

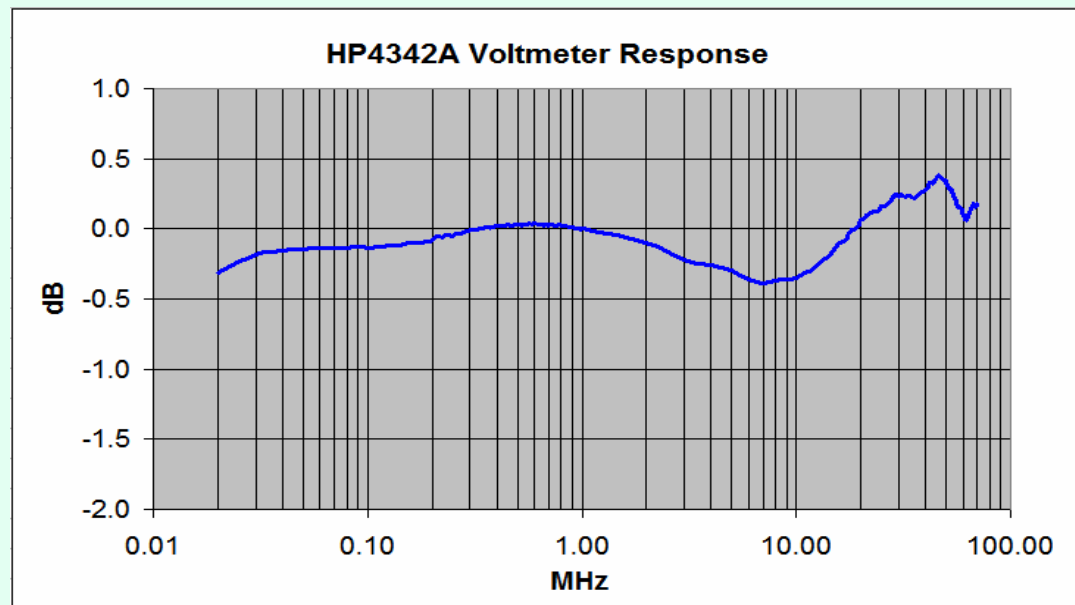

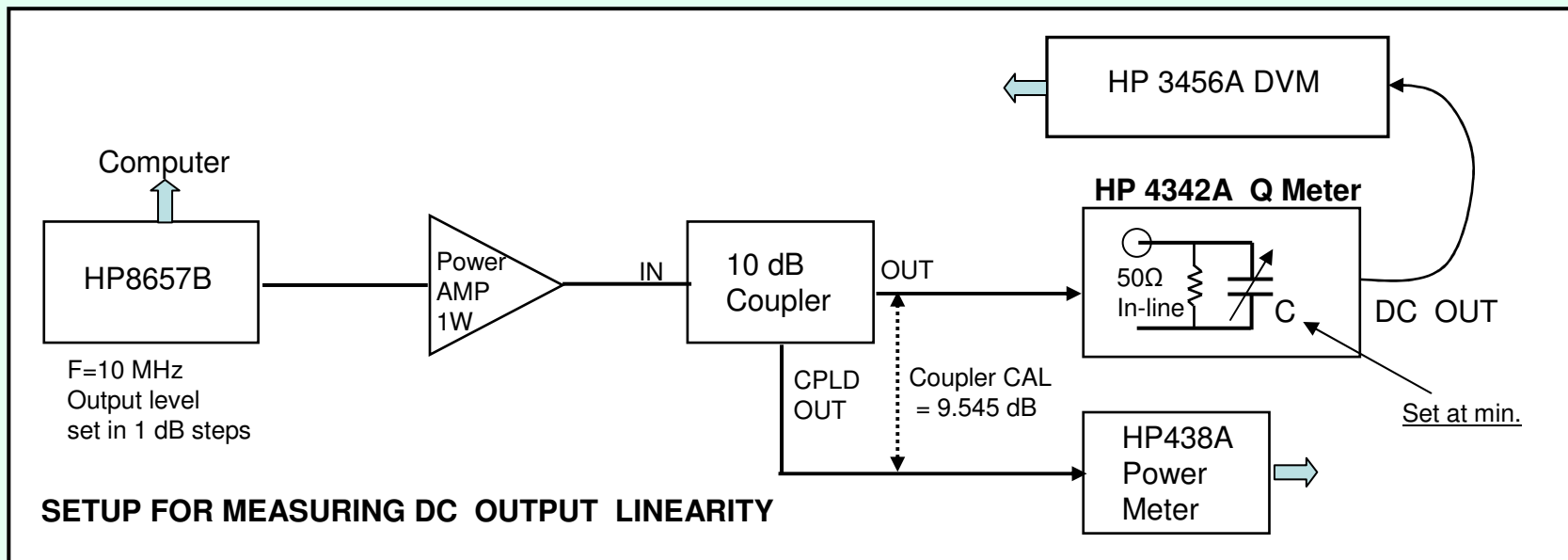
## Measuring DC Output Linearity at Q's of 500 to 2000

NOTE: A DVM connected at the Q Meter DC Output increases the resolution in Q Measurements and allows measuring Q's above 1000. Insure the DC output is properly calibrated.





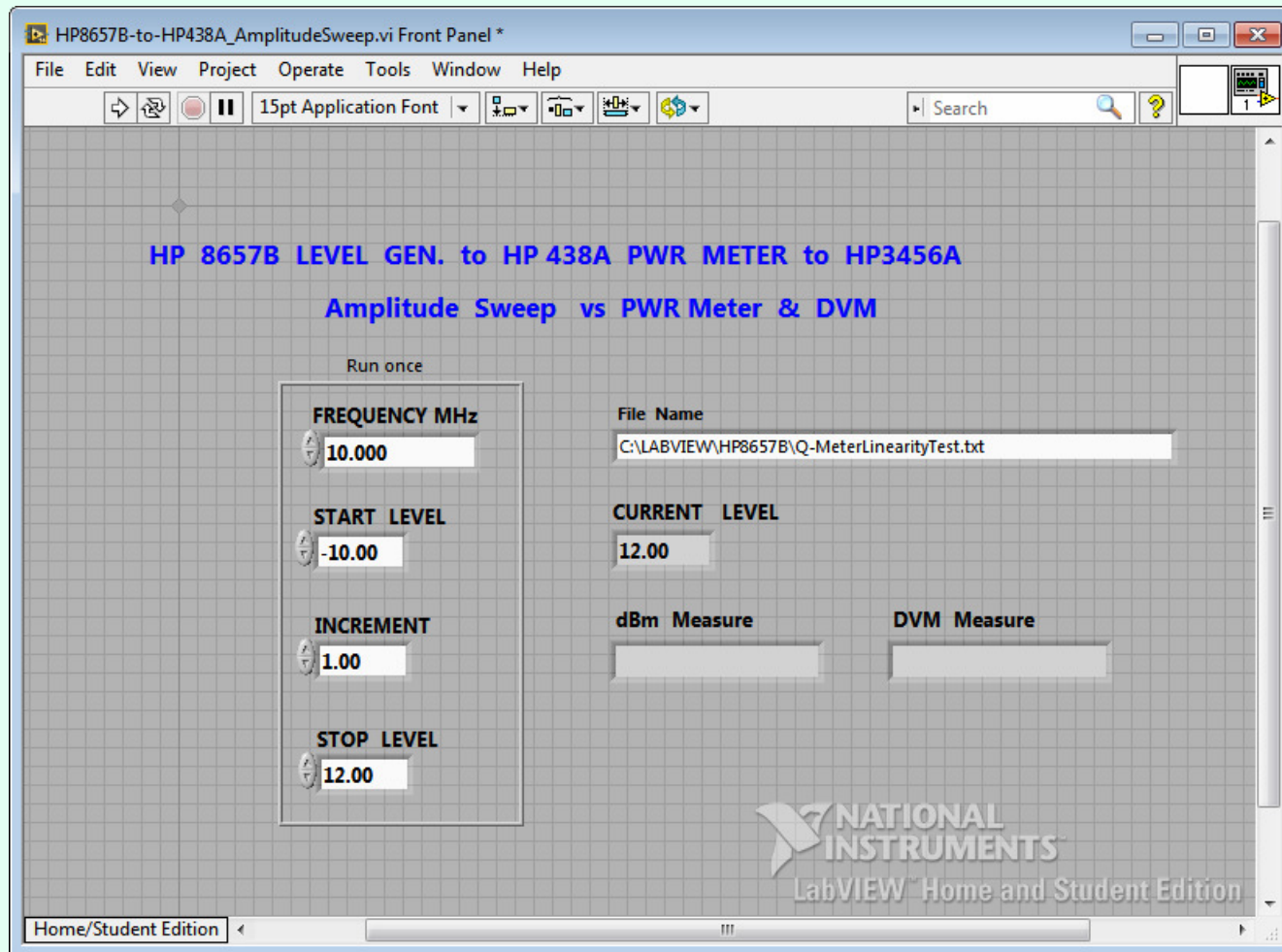
## Measuring DC Output Linearity at Q's of 500 to 2000 Using Labview to automate the measurements



## Measured DC Output Linearity

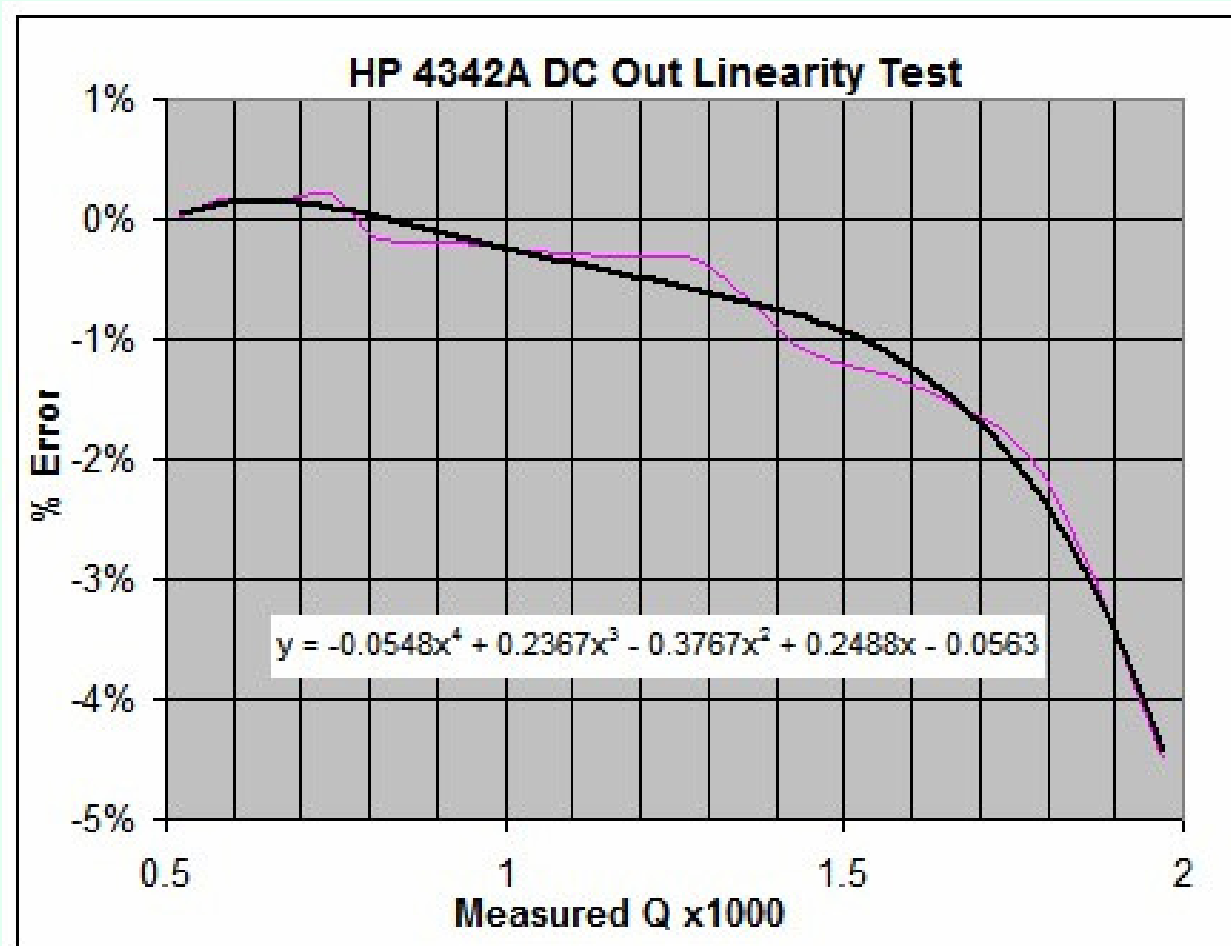

## **Measuring the HI Z Buffer Input Resistance ( $R_p$ )**

Requires another Q meter, using delta Q mode for this measurement !

## Building my own Transformer

50:1 ratio needed: 50 turns and 1 turn will be used.

T68-6 Iron powder core provides  $L = 12 \mu\text{H}$  with 51 turns.

This will give -3 dB point at: 33 KHz when driven with a source resistance of 2.5 ohms.





$$F_{-3\text{dB}} = 2.5 / (2 \cdot \pi \cdot L)$$

T68-6 frequency range is OK. #30 AWG wire is OK

The screenshot shows the 'mini Ring Core Calculator 1.2' window. The 'Ferroxcube' tab is selected, with 'Iron Powder T .. - ..' chosen. The core type is 'T68' with 6 turns, and the permeability  $\mu_i$  is 8. The frequency range is set to '2 - 50 MHz'. The core dimensions are OD: 0.690 in, ID: 0.370 in, and h: 0.190 in. The inductance is 12  $\mu\text{H}$ , the number of turns is 51, the length of the wire is 2.986 ft, and the maximum diameter of the wire is #24 AWG. The application section shows a frequency of 0.033 MHz, resulting in  $X_L = 2.488 \Omega$ . The voltage is 0 V, and the core loss is 0 mW/cm<sup>3</sup>. The temperature rise is 0 °C. The supplier is listed as AMIDON.


Parameter	Value
Core Type	T68
Turns	6
Permeability ( $\mu_i$ )	8
Frequency Range	2 - 50 MHz
OD (in)	0.690
ID (in)	0.370
h (in)	0.190
Inductance	12 $\mu\text{H}$
Turns	51
Length (wire)	2.986 ft
max. D (wire)	#24 AWG
Frequency	0.033 MHz
$X_L$	2.488 $\Omega$
Voltage	0 V
Core Loss	0 mW/cm <sup>3</sup>
Temperature Rise	0 °C

# Building my own Transformer

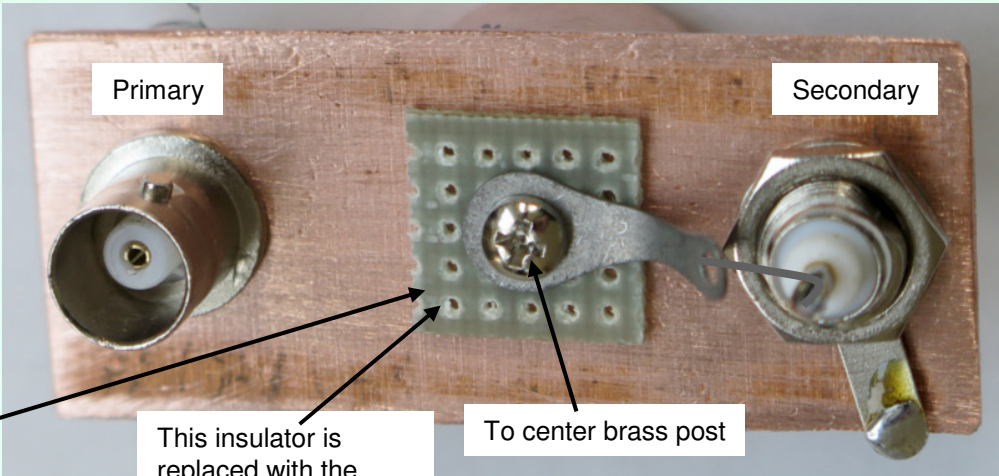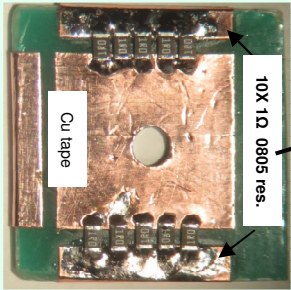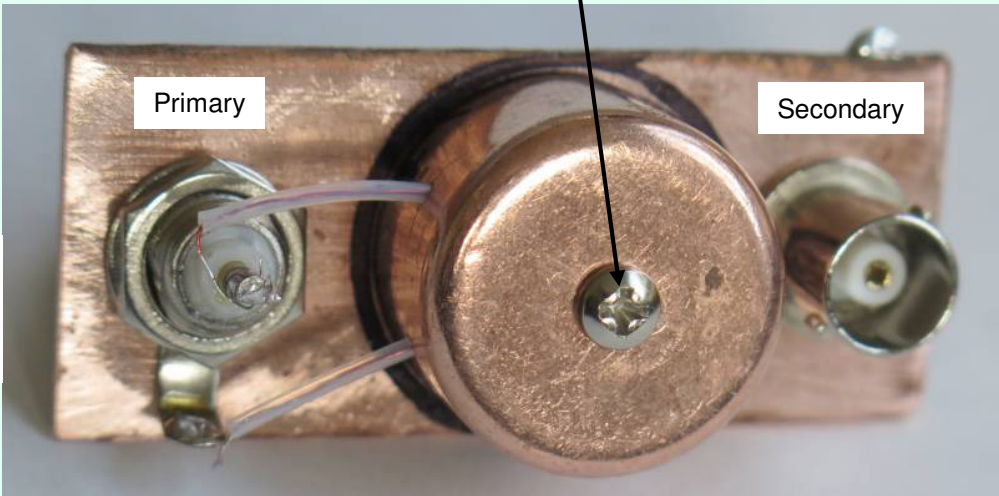
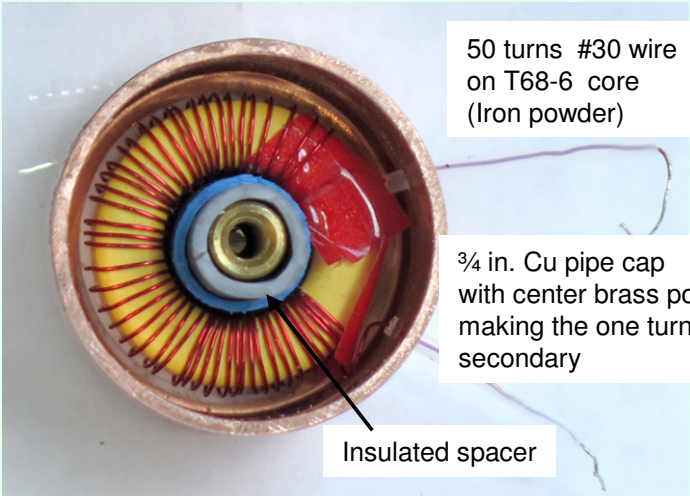


# Building my own Transformer: Frequency Response, Output Resistance and Inductance

## Frequency Response

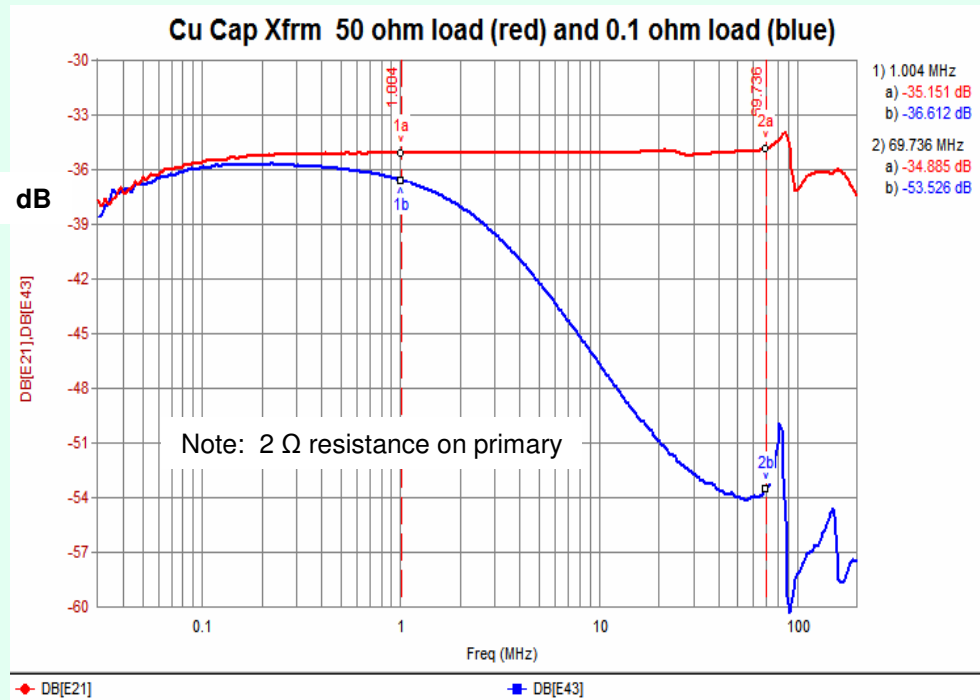

## Output Resistance and Inductance

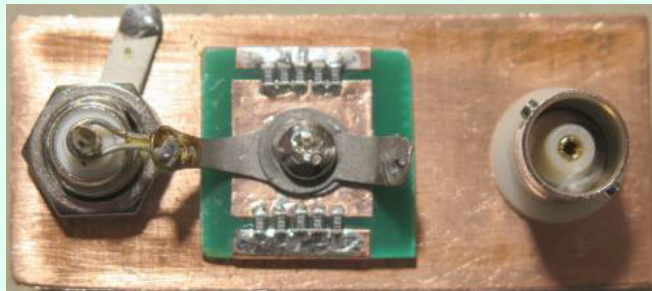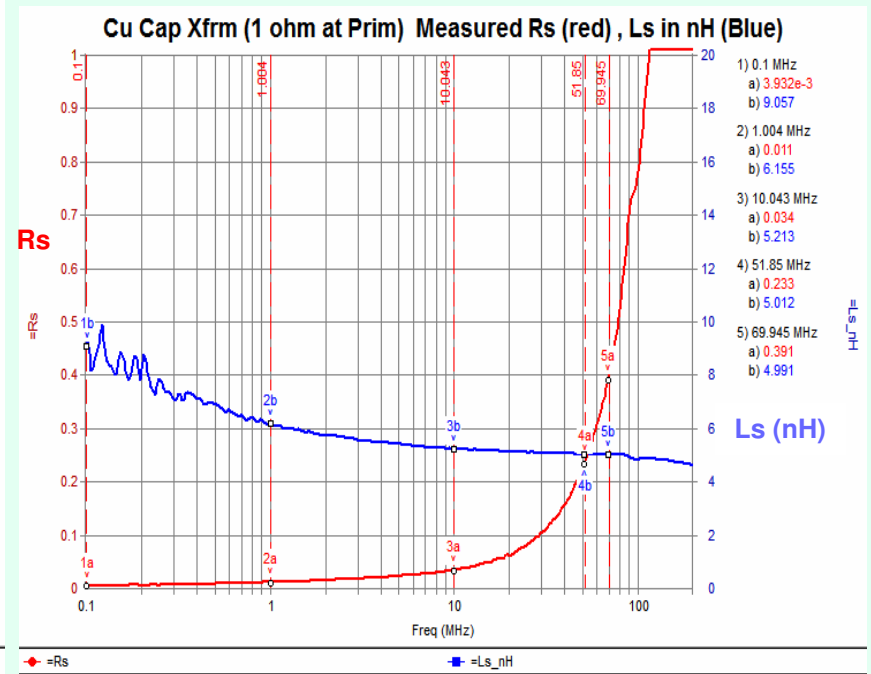


0.1  $\Omega$  load connected on the secondary

## Comparing both Transformers

The Cu Cap Transformer has ~ 2.5 times higher resistance


The equations below predict the source resistance at all frequencies and may be used to correct the measured Q.

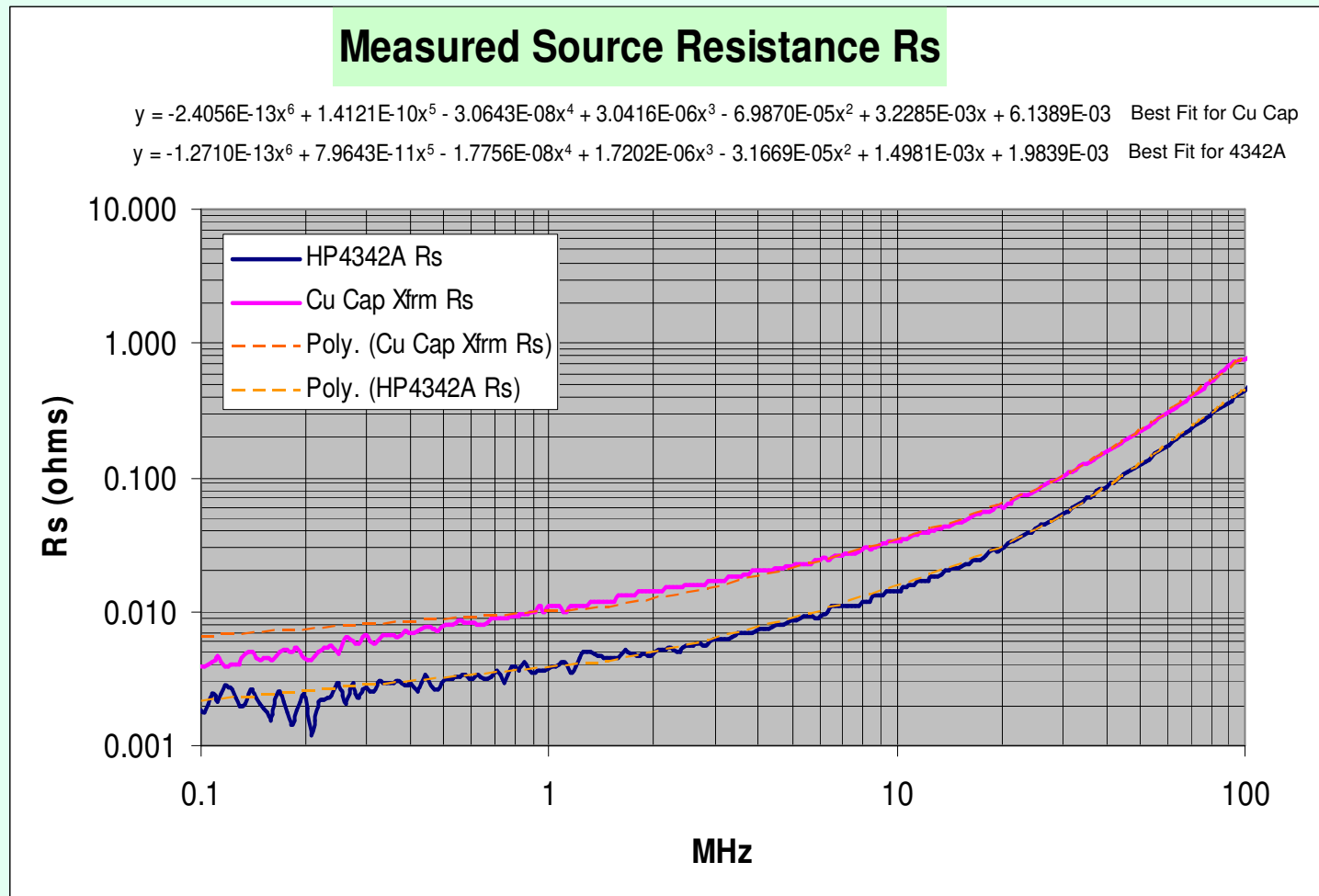See: **HP 4342A Q Meter Corrections.xls**




## Comparing both Transformers

### Measured Frequency Response

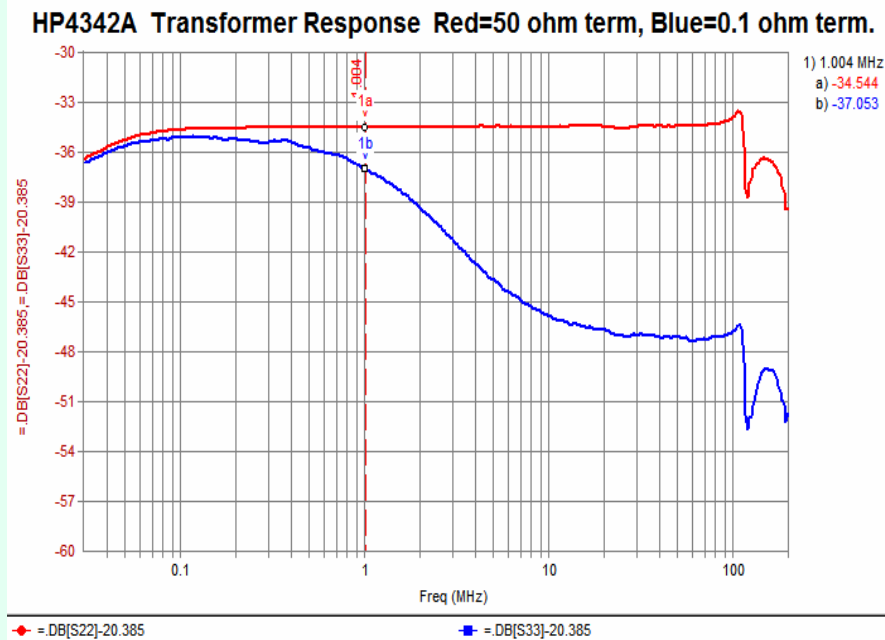

Output  $L_s$  value ~ 3 nH.

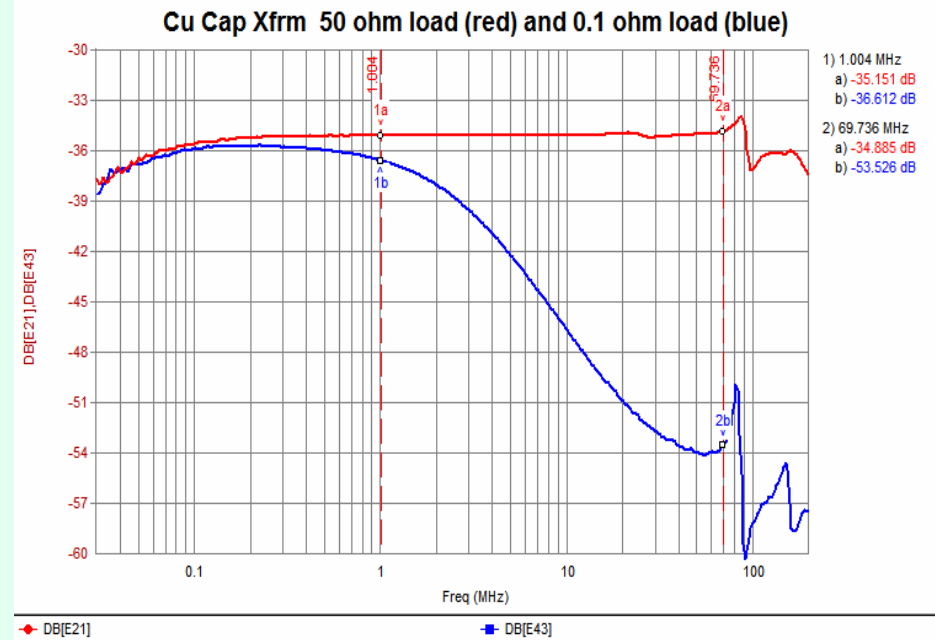

Output  $L_s$  value ~ 5 nH.

The higher source inductance  $L_s$  probably caused the increased S43 drop above 10 MHz



## Building my own Transformer - Improved Version ?

Using a smaller core,  $\mu = 10$  instead of 8, and a smaller pipe cap might help to increase coupling...  
And provide a lower source resistance  $R_s$ .

**Called the V2 transformer**

mini Ring Core Calculator 1.2

Info Tools Language (Sprache) Units Help

$R_s$   $\mu$  Cu inf ?

Ferroxcube Unknown Cores Air Cores  
Iron Powder T .. .. Ferrite FT .. .. SIFFERIT

T50 2 Color Frequency Range  
 $\mu = 10$  1 - 30 MHz

AL = 4.9 nH/N<sup>2</sup>

OD 0.500 in ID 0.303 in h 0.190 in

Inductance Turns Length (wire) max. D (wire)  
12 μH 49 2.362 ft # 25 AWG

Application

Frequency 0.033 MHz => XL = 2.488 Ω max. Flux xxx G


Voltage 0 V Flux 0 G

Core Loss 0 mW/cm<sup>3</sup> 0 W Temperature Rise 0 °C

Calculating inductance by number of turns

N 0.000 H XL = 0.000 Ω

Supplier: AMIDON

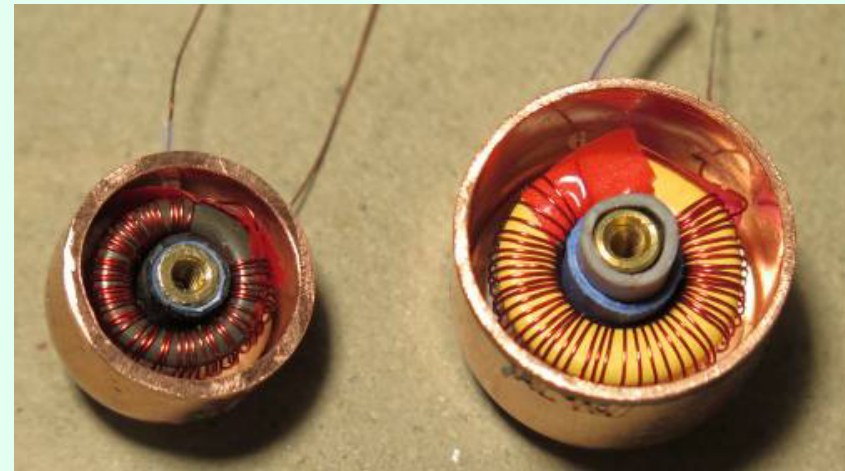


**1/2 in. pipe cap**  
T50-2 core  
AWG 30 wire  
**V2 transformer**  
# turns=51  
L-13.7 μH  
Q=15 @ 100 KH  
65 mil plastic spacer  
at bottom & top

**3/4 in. pipe cap**  
T68-6 core  
AWG 30 wire  
# turns=50  
L-13.1 μH  
Q=13 @ 100 KHz  
65 mil plastic spacer  
at bottom & top


## V2 Transformer Tests

### Frequency Response

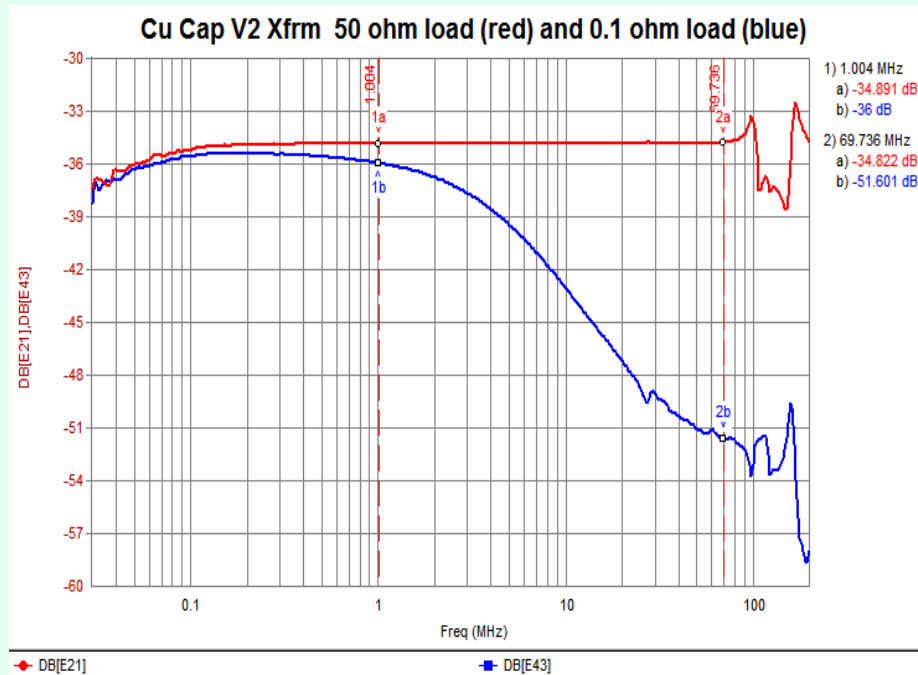

Very flat frequency response up to 70 MHz with 50Ω load  
Response with 0.1 ohm is improved compared to previous xfrm.  
But worse compared to HP4342A.


### Output Resistance and Inductance

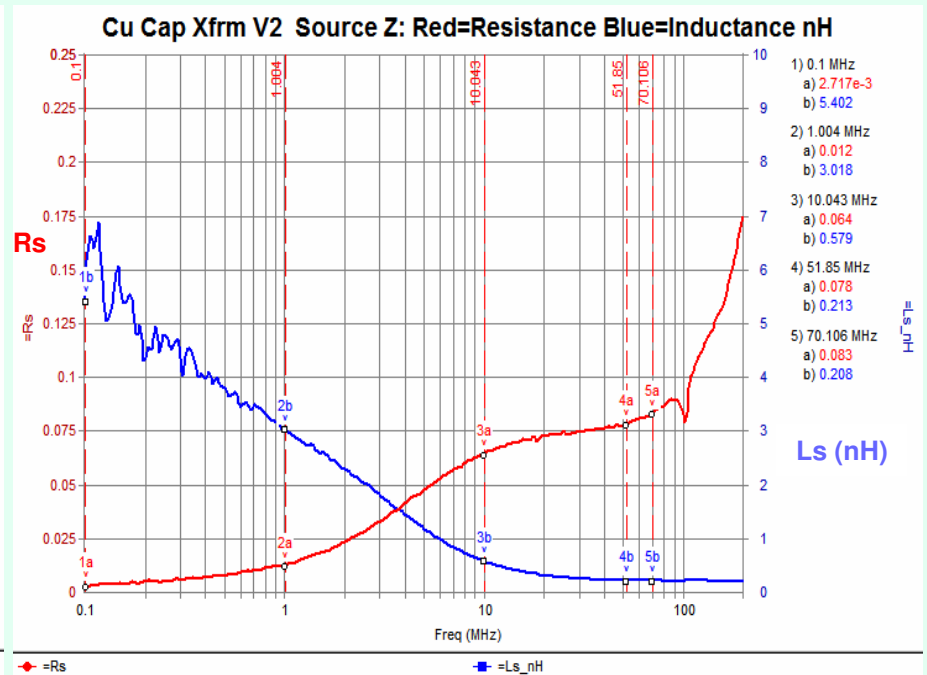

Output Ls value very low ~0.6 nH @ 10 MHz  
Rs is ~ 80 mΩ from 10 to 70 MHz
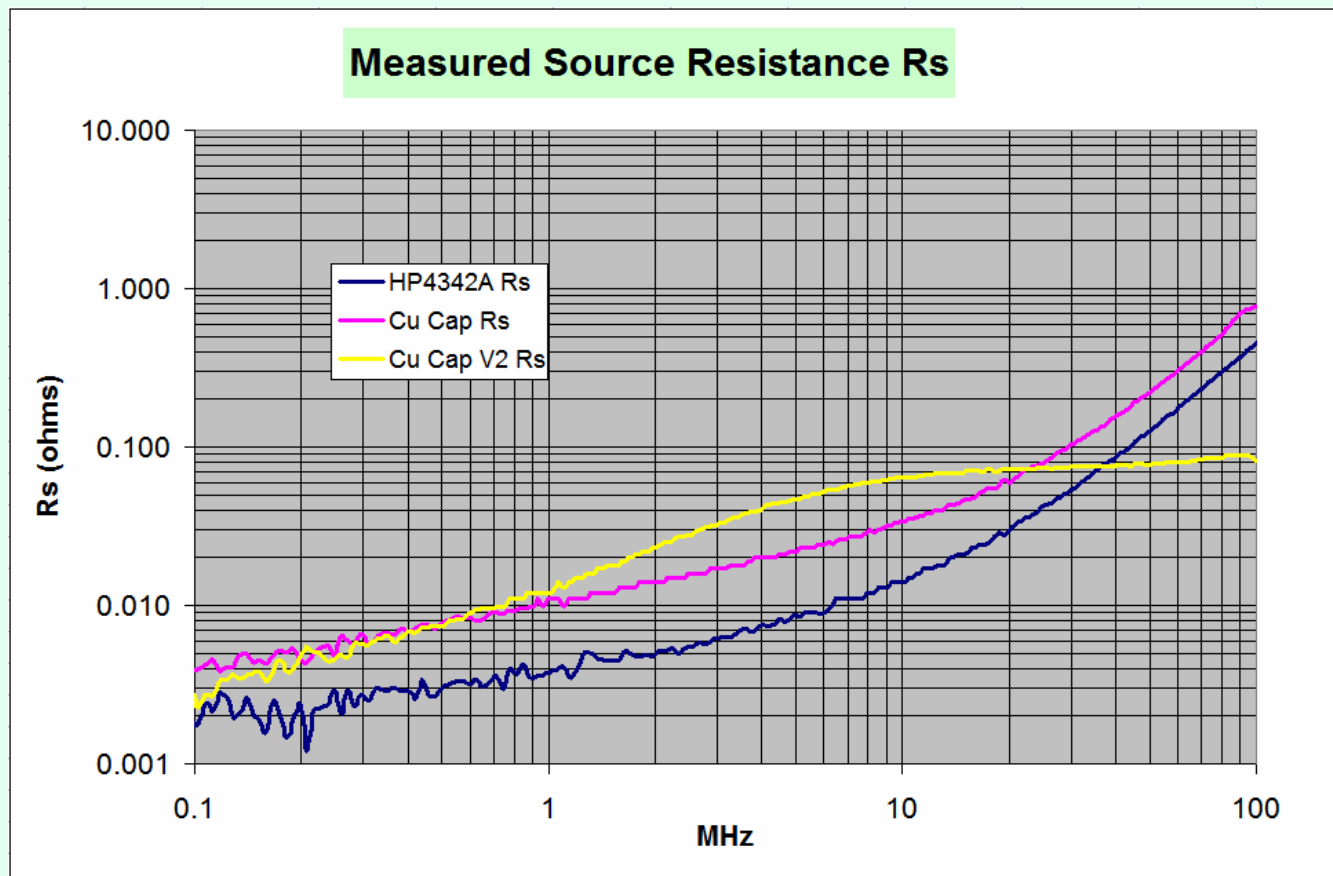
## All 3 Transformers Compared

HP documentation only mentions about 1 milliohm source resistance.  
But the source resistance  $R_s$  goes up with frequency by a factor of 200 at 70 MHz, as shown below.  
It is then important to apply proper corrections for the rising source resistance especially above 10 MHz.



## Correcting the Q readings on the HP4342A


For the Source Resistance  $R_s$  and  $L_s$  values plus

Tuning Capacitor residual Inductance and Voltmeter parallel  $R_p$

Ref: HP 4342A – Boonton 260A Q Meter Corrections1.xls

Q Factor Rs , Ls and Lc Corrections for the HP4342A Q Meter								Jacques Audet	
Ref: Q Factor Corrections for the source resistance.xmcd								VE2AZX	Dec-22
Required Data			Resonating Capacitor Residual Inductance Lc= 0.00122 μH					Rev 4 Feb 17 2023	
Ls = source Inductance (μH) Ls= 0.003 μH									
			Calculations			Calculations			
Frequency	Q	Capacitance	Reactance	HP4342A	Corrected	Corrected	Corrected	Inductor	Voltmeter Rp
MHz	Reading	pF	ohms	Rs Curve	Q Reading	Inductance μH	Resonant Fr MHz	ESR Ω	Curve MΩ
0.1	300	1000	1591.5	0.002	302.9	2533.025	0.1000	5.254	51.331
1	1000	400	397.9	0.003	1017.5	63.322	1.0000	0.391	46.459
10	400	400	39.7	0.015	473.0	0.629	10.0335	0.084	17.139
20	300	300	26.4	0.030	458.0	0.207	20.2030	0.057	5.660
30	200	200	26.3	0.052	331.6	0.137	30.4602	0.079	1.869
40	100	100	39.5	0.084	127.1	0.154	40.5440	0.309	0.617
48.82	200	100	32.2	0.119	855.1	0.102	49.8191	0.037	0.232

## HP 4342A Source Q factor vs Frequency

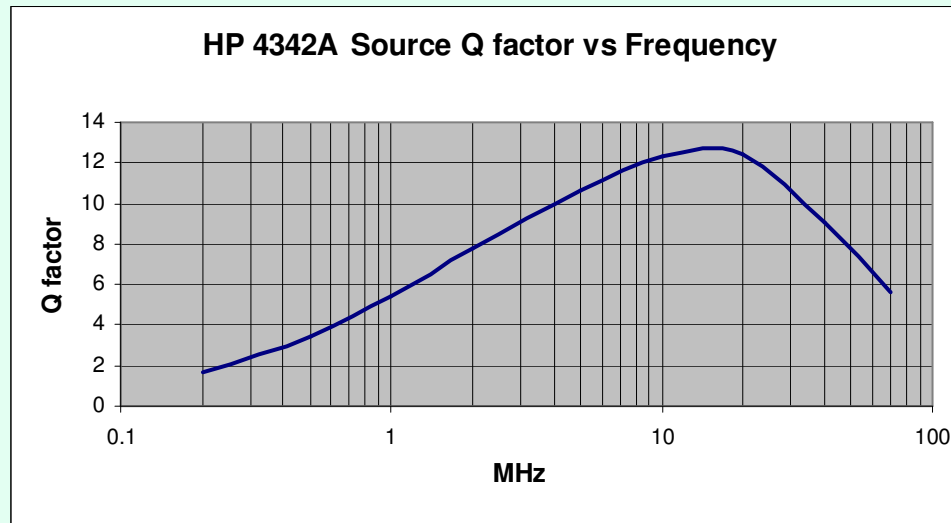

Measuring the RF voltage at the transformer output is not a good idea because its output impedance is not purely resistive.

**The source impedance is more reactive than resistive.** (At 10 MHz the measured Q is over 12).

This means that the source reactance will decrease the apparent source voltage when the coil ESR is low.

An auto leveling circuit at the transformer output will increase the drive voltage by a factor of 1 to 12 approx, which will throw out the Q measurement accuracy completely.

Note that the source inductance is small (3 nH) and that it only adds to the coil inductance being measured.

Only the source resistance will degrade the Q factor. HP documentation only mentions about 1 milliohm source resistance.

But the source resistance  $R_s$  goes up with frequency by a factor of 200 at 70 MHz, as I measured.

It is then important to apply proper corrections for the rising source resistance especially above 10 MHz.


This document summarizes the tests that I did on the HP4342A: [http://ve2azx.net/technical/HP4342A\\_Q%20Meter\\_Tests1.pdf](http://ve2azx.net/technical/HP4342A_Q%20Meter_Tests1.pdf)

It is much better to correct the Q readings.


Here is an Excel file that will help in doing the corrections:

[http://ve2azx.net/technical/HP4342A\\_%20Boonton\\_260A\\_Q\\_Meter\\_Corrections.xls](http://ve2azx.net/technical/HP4342A_%20Boonton_260A_Q_Meter_Corrections.xls)
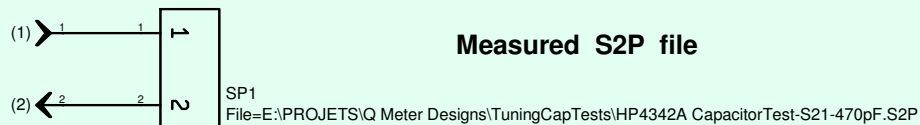
# HP 4342A Tuning Capacitor Residual Inductance, using S21 measurement



Measured S2P file

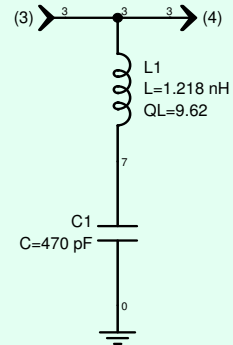



Equivalent Circuit

L1 is adjusted to obtain the same resonant frequency. (210.56 MHz)

**L1 = 1.22 nH** quite a low value !

QL is adjusted to obtain the same S43 depth, as with S21

C1 is the tuning capacitor

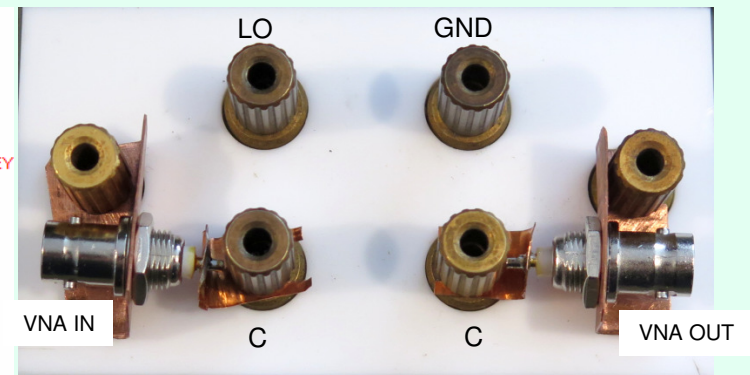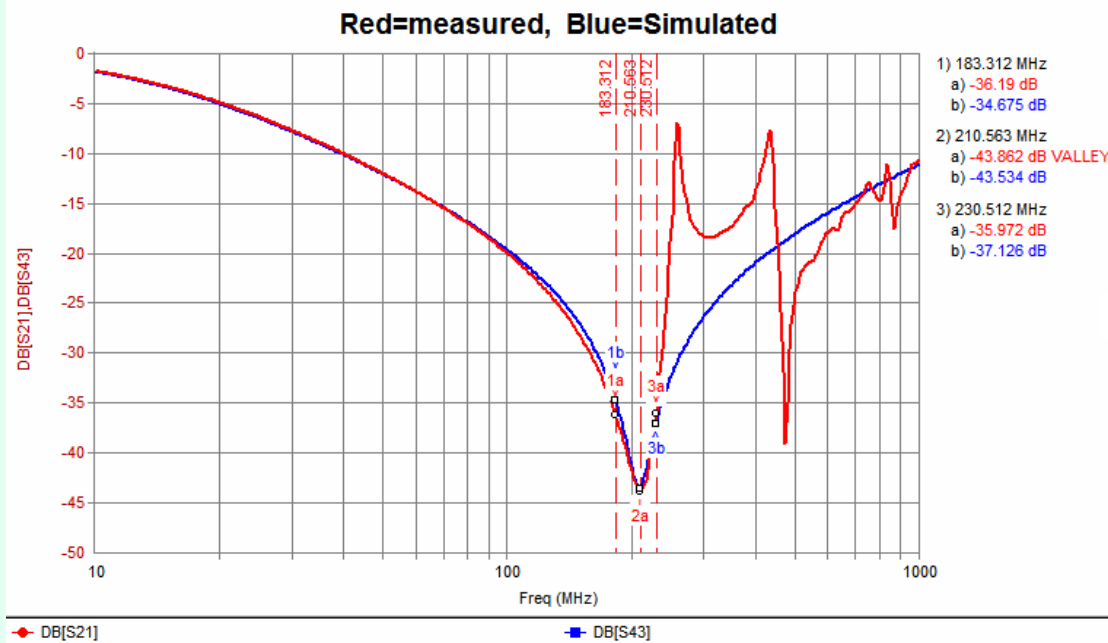

## Q METER BASIC CALCULATIONS

f := 1 C := 20 Q := 1000 Zs1 := 0.004 f in MHz, C in pF, Q factor, Zs1 = Measured transfo series resistive impedance @ f (MHz)

$$XC := \frac{10^6}{2 \cdot \pi \cdot f \cdot C} \quad XC = 7.958 \times 10^3 \quad \text{Capacitive reactance of capacitor C}$$

$$Rp := Q \cdot XC = 7.958 \times 10^6 \quad \text{Tuned circuit Parallel Resistance}$$

$$Zp := 100 \cdot Rp = 7.958 \times 10^8 \quad \text{Impedance Converter Parallel Resistance for 1% error}$$

$$Rs := \frac{XC}{Q} = 7.958 \quad \text{Tuned circuit Series Resistance}$$

$$Zs := \frac{Rs}{100} = 0.07958 \quad \text{One turn transformer secondary highestest Series Impedance for 1% error}$$

$$Pe := \frac{100 \cdot Zs1}{Rs + Zs1} = 0.05 \quad \text{Percent uncorrected error from the transformer secondary Impedance}$$

f := 1 C := 450 Q := 1000 Zs1 := 0.004 f in MHz, C in pF, Q factor, Zs1 = Measured transfo series resistive impedance @ f (MHz)

$$XC := \frac{10^6}{2 \cdot \pi \cdot f \cdot C} \quad XC = 353.678 \quad \text{Capacitive reactance of capacitor C}$$

$$Rp := Q \cdot XC = 3.537 \times 10^5 \quad \text{Tuned circuit Parallel Resistance}$$

$$Zp := 100 \cdot Rp = 3.537 \times 10^7 \quad \text{Impedance Converter Parallel Resistance for 1% error}$$

$$Rs := \frac{XC}{Q} = 0.354 \quad \text{Tuned circuit Series Resistance}$$

$$Zs := \frac{Rs}{100} = 3.537 \times 10^{-3} \quad \text{One turn transformer secondary highestest Series Impedance for 1% error}$$

$$Pe := \frac{100 \cdot Zs1}{Rs + Zs1} = 1.118 \quad \text{Percent uncorrected error from the transformer secondary Impedance}$$

f := 50 C := 20 Q := 500 Zs1 := 0.130 f in MHz, C in pF, Q factor, Zs1 = Measured transfo series resistive impedance @ f (MHz)

$$XC := \frac{10^6}{2 \cdot \pi \cdot f \cdot C} \quad XC = 159.155 \quad \text{Capacitive reactance of capacitor C}$$

$$Rp := Q \cdot XC = 7.958 \times 10^4 \quad \text{Tuned circuit Parallel Resistance}$$

$$Zp := 100 \cdot Rp = 7.958 \times 10^6 \quad \text{Impedance Converter Parallel Resistance for 1% error}$$

$$Rs := \frac{XC}{Q} = 0.318 \quad \text{Tuned circuit Series Resistance}$$

$$Zs := \frac{Rs}{100} = 3.1831 \times 10^{-3} \quad \text{One turn transformer secondary highestest Series Impedance for 1% error}$$

$$Pe := \frac{100 \cdot Zs1}{Rs + Zs1} = 28.998 \quad \text{Percent uncorrected error from the transformer secondary Impedance}$$

f := 50 C := 100 Q := 500 Zs1 := 0.130 f in MHz, C in pF, Q factor, Zs1 = Measured transfo series resistive impedance @ f (MHz)

$$XC := \frac{10^6}{2 \cdot \pi \cdot f \cdot C} \quad XC = 31.831 \quad \text{Capacitive reactance of capacitor C}$$

$$Rp := Q \cdot XC = 1.592 \times 10^4 \quad \text{Tuned circuit Parallel Resistance}$$


$$Zp := 100 \cdot Rp = 1.592 \times 10^6 \quad \text{Impedance Converter Parallel Resistance for 1% error}$$

$$Rs := \frac{XC}{Q} = 0.064 \quad \text{Tuned circuit Series Resistance}$$

$$Zs := \frac{Rs}{100} = 6.3662 \times 10^{-4} \quad \text{One turn transformer secondary highestest Series Impedance for 1% error}$$

$$Pe := \frac{100 \cdot Zs1}{Rs + Zs1} = 67.127 \quad \text{Percent uncorrected error from the transformer secondary Impedance}$$
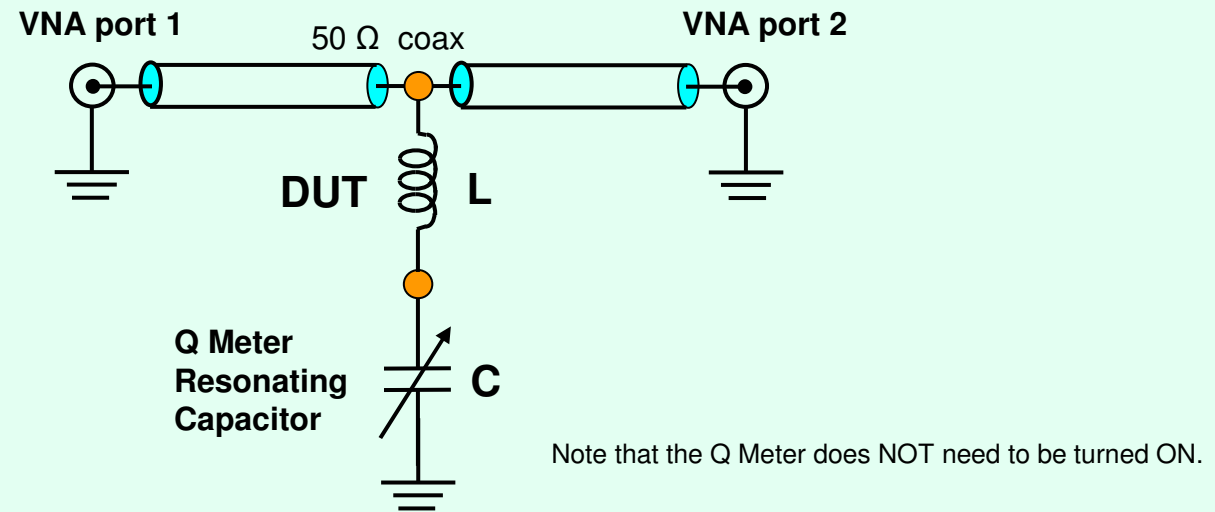
## The Transmission Method for Measuring the Q Factor




Calculations are used to derive the R, L and C components as seen from the three insertion loss measurements.  
(R is the ESR associated with the inductor)

This means that the additional inductance of the connecting wires of the L and C components is taken into account in the Q measurement.





## The Transmission Method

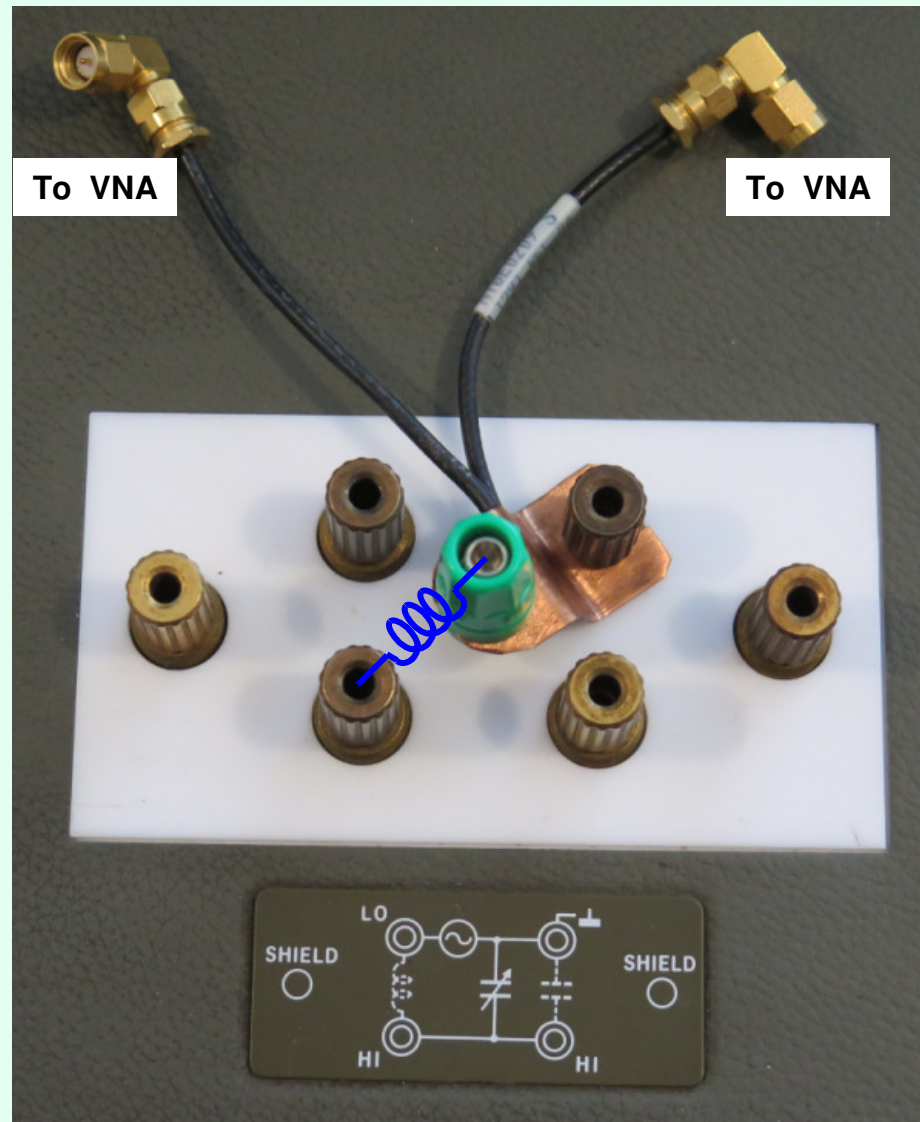
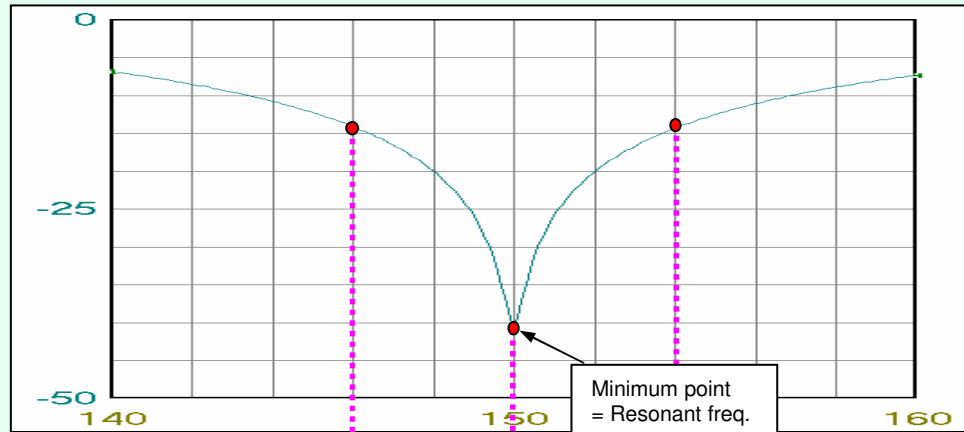
# The Transmission Method

See: [http://ve2azx.net/technical/Calc\\_Series-Par\\_RLC.xls](http://ve2azx.net/technical/Calc_Series-Par_RLC.xls)



DATA ENTRY		FREQUENCY (MHz)	7.079	7.118	7.156	GENERATOR / DETECTOR		IMPEDANCE (ohms)	50		
ZONE		LOSS (dB)	19.935	28.297	20.023			Loss values in dB obtained after zeroing with RLC components removed.			
SERIES MODE RESULTS			Q FACTOR =			223.53	PARALLEL MODE RESULTS				
			3 dB BANDWIDTH (KHz)			32					
SERIES Ls in nH		4999.66	CALC. RESONANT FREQ in MHz			7.1176	PARALLEL Lp nH		250.02		
SERIES Cs in pF		100.01	% OFF FROM MEAS. RESONNANCE			-0.005	PARALLEL Cp pF		1999.86		
SERIES Rs ohms		1.000	Comments zone						PARALLEL Rp ohms		2499.3
SERIES Xs ohms		223.592							PARALLEL Xp ohms		11.181

An error of 0.1 dB will give give about 1% error in the calculated Q  
(Tested with Q around 220)