

Ferrite Z vs SWR as measured in test fixture with 50 ohm shunt resistor

J. Audet
Oct. 2014

Z₀ = Fixture shunt resistor (50 ohms)
 Z = Effective resistive impedance across bridge = RL in parallel with Z₀
 RL = Resistance across Z₀ giving a specific SWR value
 XL = Reactance across Z₀ giving a specific SWR value
 CR = Coeff of reflection
 SWR = SWR value measured.

CASE WHERE RL IS RESISTIVE SWR calculation with Z₀ in parallel with RL

$$\text{SWR} = \frac{1 + |\text{CR}|}{1 - |\text{CR}|} \quad \text{Eq 1 SWR vs CR (coeff of reflection)}$$

$$\text{CR} = \frac{Z - Z_0}{Z + Z_0} \quad \text{Eq 2 CR vs Z (unknown impedance) and } Z_0 \text{ (ref. impedance = 50)}$$

$$Z = \frac{\text{RL} \cdot Z_0}{\text{RL} + Z_0} \quad \text{Eq 3 The effective Z consists of RL (unknown) and } Z_0 \text{ in parallel}$$

$$\text{SWR} = \frac{1 + |\text{CR}|}{1 - |\text{CR}|} \quad \text{Eq 1 repeated}$$

$$\text{SWR} = \frac{\left(1 + \frac{|Z - Z_0|}{|Z + Z_0|}\right)}{\left(1 - \frac{|Z - Z_0|}{|Z + Z_0|}\right)} \quad \text{Eq 4: substitute Eq 2 into Eq 1}$$

$$\text{SWR} = \frac{\left[1 + \frac{\left|\text{RL} \cdot \frac{Z_0}{(\text{RL} + Z_0)} - Z_0\right|}{\left|\text{RL} \cdot \frac{Z_0}{(\text{RL} + Z_0)} + Z_0\right|}\right]}{\left[1 - \frac{\left|\text{RL} \cdot \frac{Z_0}{(\text{RL} + Z_0)} - Z_0\right|}{\left|\text{RL} \cdot \frac{Z_0}{(\text{RL} + Z_0)} + Z_0\right|}\right]} \quad \text{Eq 5: sub. Eq 3 into Eq 4}$$

$$\text{SWR} = \frac{\left[-Z_0 \cdot (2 \cdot \text{RL} + Z_0) + Z_0^2\right]}{\left[-Z_0 \cdot (2 \cdot \text{RL} + Z_0) + Z_0^2\right]} \quad \text{Eq 6 Simplify Eq 5}$$

$$\text{RL} = \frac{Z_0}{(\text{SWR} - 1)} \quad \text{Eq 7 Solve for RL in Eq 6}$$

CASE WHERE RL IS REACTIVE = XL
SWR calculation with Zo in parallel with XL

$$SWR = \frac{1 + |CR|}{1 - |CR|} \quad \text{Eq 1 SWR vs CR (coeff of reflection)}$$

$$CR = \frac{Z - Z_0}{Z + Z_0} \quad \text{Eq 2 CR vs Z (unknown impedance) and } Z_0 \text{ (ref. impedance = 50)}$$

$$Z = \frac{j \cdot XL \cdot Z_0}{j \cdot XL + Z_0} \quad \text{Eq 8 The effective Z consists of XL (unknown) and } Z_0 \text{ in parallel}$$

$$CR = \frac{Z - Z_0}{Z + Z_0} \quad \text{Eq 2 repeated}$$

$$CR = \frac{\left[i \cdot XL \cdot \frac{Z_0}{(i \cdot XL + Z_0)} - Z_0 \right]}{\left[i \cdot XL \cdot \frac{Z_0}{(i \cdot XL + Z_0)} + Z_0 \right]} \quad \text{Eq 9: Eq 8 into Eq 2}$$

$$CR = \frac{-Z_0}{(2i \cdot XL + Z_0)} \quad \text{Eq 10: Eq 9 simplified}$$

$$SWR = \frac{1 + |CR|}{1 - |CR|} \quad \text{Eq 1 repeated}$$

$$SWR = \frac{\left(1 + \frac{|Z_0|}{\sqrt{Z_0^2 + 4 \cdot XL^2}} \right)}{\left(1 - \frac{|Z_0|}{\sqrt{Z_0^2 + 4 \cdot XL^2}} \right)} \quad \text{Eq 11: Eq 10 into Eq 1}$$

$$SWR = \frac{\left(\sqrt{Z_0^2 + 4 \cdot XL^2} + |Z_0| \right)}{\left(\sqrt{Z_0^2 + 4 \cdot XL^2} - |Z_0| \right)} \quad \text{Eq 12: Eq 11 simplified}$$

$$\left[\begin{array}{l} \frac{1}{2} \cdot \sqrt{-Z_0^2 + \frac{(-SWR \cdot |Z_0| - |Z_0|)^2}{(SWR - 1)^2}} \\ \frac{-1}{2} \cdot \sqrt{-Z_0^2 + \frac{(-SWR \cdot |Z_0| - |Z_0|)^2}{(SWR - 1)^2}} \end{array} \right]$$

Solving for XL:
 We use the positive root

$$XL = \frac{1}{2} \cdot \sqrt{-Z_0^2 + \frac{(-SWR \cdot Z_0 - Z_0)^2}{(SWR - 1)^2}} \quad \text{Eq 13}$$


$$XL = \frac{4 \cdot SWR \cdot Z_0^2}{(SWR - 1)^2} \quad \text{Eq 14: Eq 13 simplified}$$

CALCULATIONS

$Z_0 := 50$ $SWR := 1.1, 1.2 \dots 6$

$$XL(SWR) := \frac{1}{2} \cdot \sqrt{\frac{4 \cdot SWR \cdot Z_0^2}{(SWR - 1)^2}} \quad \text{Eq 14}$$
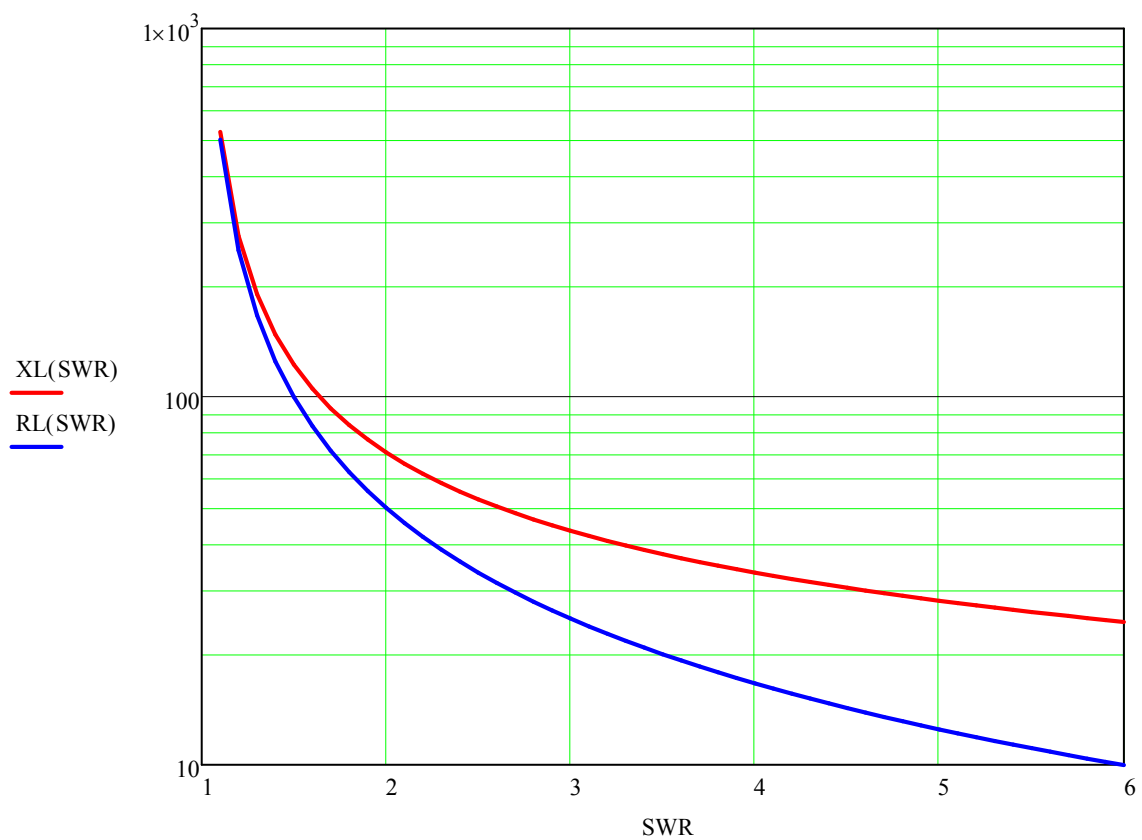
$$RL(SWR) := \frac{Z_0}{(SWR - 1)} \quad \text{Eq 7}$$



MORE CHECKS

X := 50 Resistance across 50 ohm termination

$$Z := \frac{50 \cdot X}{50 + X} \quad \text{Eq 1} \quad Z = 25 \quad |Z| = 25$$

$$\text{CR} := \frac{Z - 50}{Z + 50} \quad \text{Eq 2} \quad \text{CR} = -0.333$$

$$\text{SWR} := \frac{1 + |\text{CR}|}{1 - |\text{CR}|} \quad \text{Eq 3} \quad \text{SWR} = 2$$

X := j·70 Reactance across 50 ohm termination

$$Z := \frac{50 \cdot X}{50 + X} \quad \text{Eq 1} \quad Z = 33.108 + 23.649i \quad |Z| = 40.687$$

$$\text{CR} := \frac{Z - 50}{Z + 50} \quad \text{Eq 2} \quad \text{CR} = -0.113 + 0.317i$$

$$\text{SWR} := \frac{1 + |\text{CR}|}{1 - |\text{CR}|} \quad \text{Eq 3} \quad \text{SWR} = 2.014$$