

## Series to Parallel Conversions

Jacques Audet VE2AZX

$R_s$ ,  $L_s$ ,  $C_s$  = Series Resistance, Inductance, Capacitance, all connected in series.

$R_p$ ,  $L_p$ ,  $C_p$  = Parallel resistance, Inductance, Capacitance, all connected in parallel.

Q is the quality factor. It is identical for the series or parallel networks.

$$R_p = R_s \cdot (1 + Q^2)$$

$$X_p = X_s \cdot \frac{1 + Q^2}{Q^2}$$

$X_s$ ,  $X_p$  = are series reactance and parallel reactances respectively.  
The parallel reactance is in parallel with  $R_p$ .

$$L_p = L_s \cdot \frac{1 + Q^2}{Q^2}$$

$$C_p = C_s \cdot \frac{Q^2}{1 + Q^2}$$

**There are many ways to calculate the Q factor:**

$$Q = \frac{X_s}{R_s} = \frac{R_p}{X_p} = \frac{\omega \cdot L_s}{R_s} = \frac{R_p}{\omega \cdot L_p} = \frac{1}{\omega \cdot C_s \cdot R_s} = R_p \cdot \omega \cdot C_p$$

Where  $\omega = 2 \cdot \pi \cdot f$  and  $f$  = frequency in Hz

For a given frequency, there is always a unique equivalent parallel circuit, and vice versa.

Impedances are generally expressed as series components unless noted otherwise.

### Example of calculation of the parallel values

Measured Impedance values:

$$R_s := 25 \ \Omega \quad L_s := 10^{-6} \ \text{H} \quad (1 \mu\text{H}) \quad f := 1 \cdot 10^6 \quad (1 \text{MHz})$$

The Q factor is calculated first:

$$Q := \frac{2 \cdot \pi \cdot f \cdot L_s}{R_s} = 0.251$$

The parallel values are calculated:

$$R_p := R_s \cdot (1 + Q^2) = 26.579$$

$$L_p := L_s \cdot \frac{1 + Q^2}{Q^2} = 1.683 \times 10^{-5} \ \text{H} \quad \text{or } 16.83 \ \mu\text{H}$$

### NOTES

Conversion to parallel is useful when the device under test is known to be a parallel circuit.  
Example: a parallel L-C circuit.

The impedance value is normally given using the series components:  $R_s + jX_s$